

# ECE 100: Linear Electronic Systems

Professor: Drew Hall

## Lab 4: Differentiator Op-Amp Circuit

Andy Tu

PID:A17650683

10/13/2023

# Table of Contents

<b>Abstract.....</b>	<b>4</b>
<b>Experimental Procedure.....</b>	<b>5</b>
Figure 1: Schematic of Differentiator Circuit.....	5
Section 1: System Level Design.....	6
Part 1).....	6
Part 2).....	6
Part 3).....	6
Part 4).....	7
Part 5).....	7
Part 6).....	7
Section 2: Circuit Level Spice Simulation.....	8
Part 1).....	8
Part 2).....	8
Part 3).....	8
Section 3: Measurement.....	9
Part 1).....	9
Part 2).....	9
Part 3).....	9
<b>Results.....</b>	<b>10</b>
Section 1: System Level Design.....	10
Part 1).....	10
(a).....	10
(b).....	11
(c).....	13
Figure 1.3.1: Bode Plot of Circuit without Compensation.....	13
Figure 1.3.2: Bode Plot.....	14
Figure 1.3.3: Step Response of Circuit without Compensation.....	14
(d).....	15
Figure 1.4.1: Bode Plot of Circuit with Compensation Resistor.....	16
Figure 1.4.2:.....	16
Figure 1.4.3: Step Response of Circuit with Compensation Resistor.....	17
Figure 1.4.4: Bode Plot of Circuit with Compensation Capacitor.....	19
Figure 1.4.5: n Resistor.....	19
Figure 1.4.6: Step Response of Circuit with Compensation Capacitor.....	20
(e).....	21
Figure 1.5.1:.....	21

Figure 1.5.2:.....	21
Figure 1.5.3:.....	22
Section 2: Circuit Level Spice Simulation.....	23
Part 1).....	24
Figure 2.1.1: Schematic of Ideal Differentiator Circuit Macro Model.....	24
Figure 2.1.2: Simulation Plot of Ideal Differentiator Macro Model.....	24
Figure 2.1.3: Schematic of Differentiator Circuit with LF411.....	25
Figure 2.1.4: Simulation Plot and Trace of Differentiator with LF411.....	25
Part 2).....	26
Figure 2.2.1: Schematic of Differentiator Circuit with $RC=1.03K\Omega$ .....	26
Figure 2.2.2: Simulation Plot and Trace with $RC=1.03K\Omega$ .....	26
Figure 2.2.3: Schematic of Differentiator Circuit with $RC=720\Omega$ .....	27
Figure 2.2.4: Simulation Plot and Trace with $RC=720\Omega$ .....	27
Figure 2.2.5: Schematic of Differentiator Circuit with $RC=700\Omega$ .....	28
Figure 2.2.6: Simulation Plot and Trace with $RC=700\Omega$ .....	28
Figure 2.2.7: Schematic of Differentiator Circuit with $RC=690\Omega$ .....	29
Figure 2.2.8: Simulation Plot and Trace with $RC=690\Omega$ .....	29
Figure 2.2.9: Schematic of Differentiator Circuit with $RC=695\Omega$ .....	30
Figure 2.2.10: Simulation Plot and Trace with $RC=695\Omega$ .....	30
Figure 2.2.11: Table of Simulated Rc Values.....	31
Part 3).....	32
Figure 2.3.1: Schematic of Differentiator Circuit with $CC=50pF$ .....	32
Figure 2.3.2: Simulation Plot and Trace with $CC=50pF$ .....	32
Figure 2.3.3: Schematic of Differentiator Circuit with $CC=35pF$ .....	33
Figure 2.3.4: Simulation Plot and Trace with $CC=35pF$ .....	33
Figure 2.3.5: Schematic of Differentiator Circuit with $CC=34.5pF$ .....	34
Figure 2.3.6: Simulation Plot and Trace with $CC=34.5pF$ .....	34
Figure 2.3.7: Table of Simulated Cc Values.....	35
Section 3: Measurements.....	36
Part 1).....	36
Figure 3.1.1: Breadboard Circuit without Compensation.....	36
Figure 3.1.2: Oscilloscope Measurements without Compensation.....	36
Part 2).....	37
Figure 3.2.1: Breadboard Circuit with $RC=1.03K\Omega$ .....	37
Figure 3.2.2: Oscilloscope Measurements with $RC=1.03K\Omega$ .....	37
Figure 3.2.3: Breadboard Circuit with $RC=1.06K\Omega$ .....	39
Figure 3.2.4: Oscilloscope Measurements with $RC=1.06K\Omega$ .....	39
Figure 3.2.5: Table of Measured Rc Values.....	40
Part 3).....	41
Figure 3.3.1: Breadboard Circuit with a Compensation Capacitor.....	41
Figure 3.3.2: Oscilloscope Measurements with $CC=515pF$ .....	41

Figure 3.3.3: Oscilloscope Measurements with CC=170pF.....	43
Figure 3.3.4: Oscilloscope Measurements with CC=150pF.....	43
Figure 3.3.5: Oscilloscope Measurements with CC=68pF.....	44
Figure 3.3.6: Oscilloscope Measurements with CC=51pF.....	44
Figure 3.3.7: Oscilloscope Measurements with CC=47pF.....	45
Figure 3.3.8: Oscilloscope Measurements with CC=50.2pF.....	45
Figure 3.3.9: Table of Measured Cc Values.....	46
<b>Conclusion.....</b>	<b>47</b>
<b>MATLAB Code.....</b>	<b>48</b>
Part 1) System Level Design.....	48
1C.....	48
1D (w/ RC).....	48
1D (w/ CC).....	48
1E.....	48

# Abstract

This project aims to design a signal processing circuit that will output the time derivative of the input scaled by a desired factor. This differentiator should convert a triangle wave of 1 V<sub>pp</sub> (peak-to-peak amplitude) at 1 kHz into a square wave of  $\pm 1$  V (at 1 kHz, of course). The lab illustrates the method of adjusting  $R_c$  (Compensation Resistor) and  $C_c$  (Compensation Capacitor) to alter the output voltage. We observed that using a compensation component greatly reduced the amount of overshoot and ringing in the output waveform. This allowed for a much cleaner square wave.

# Experimental Procedure

## Tools:

- P-Spice Simulation Software
- Oscilloscope
- Function Generator ( $\geq 1$  MHz)
- DC Power Supply
- LM411 Op-Amp
- Circuit Components (Resistors, Caps, Etc.)

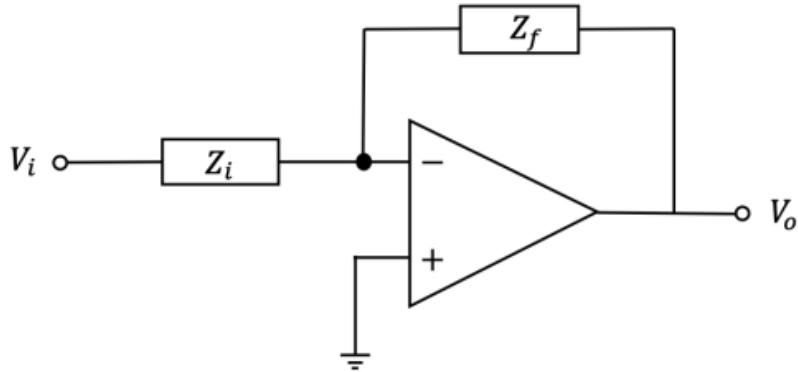


Figure 1: Schematic of Differentiator Circuit

The closed-loop gain or the transfer function for the op-amp inverter, including the frequency-dependant open-loop op-amp gain,  $a(s)$ , is:

$$H(s) = A(s) = \frac{V_o(s)}{V_{in}(s)} = \left( -\frac{Z_f(s)}{Z_i(s)} \times \frac{a(s)B(s)}{1 + a(s)B(s)} \right),$$

where  $T(s) = a(s)B(s) = a(s) \frac{Z_i(s)}{Z_i(s) + Z_f(s)}$  is the loop gain.

When the loop gain is large,  $A(s) \rightarrow \frac{-Z_f(s)}{Z_i(s)}$ , which can be called the “ideal” transfer function

because it would apply if the op-amp were ideal. The factor  $\frac{aB}{1 + aB}$  gives the deviation from ideal behavior. All feedback circuits have a factor like this in their transfer function. The possibility of having a zero in the term  $(1 + aB)$  causes instability.

## Section 1: System Level Design

### **Part 1)**

Using  $H_{ideal}(s) = \left( -\frac{Z_f(s)}{Z_i(s)} \right) = (-sRC)$  in an op-amp differentiator, we know that

$V_o(t) = \left( -RC \frac{dV_i(t)}{dt} \right)$ . We need  $V_o(t) = \pm 1V$  or  $2V_{PP}$  for a  $1V_{PP}$  triangle wave input

signal. We must choose the RC product necessary to meet the specs. A reasonable choice for the resistor is  $R = 100k\Omega$ . You can then find the required capacitor value.

### **Part 2)**

Check that R and C have correctly been calculated by simulating the differentiator circuit with an ideal op-amp. Read the Notes included in this document to learn more about finding this component. Use VPulse as the input and set the parameters to provide a few cycles for a  $1V_{PP}$  triangle wave. Make sure that the output voltage is the desired square wave. Include these plots in your report and show your work for the calculations of the capacitor value

### **Part 3)**

We can think of the differentiator as the product of  $H_{ideal}$ , which converts the triangle wave into the desired square wave, and a second filter  $H(s) = \frac{aB}{1+aB}$  which turns out to be a second-order low-pass filter. This low pass filter will have finite bandwidth and, thus, finite rise time. We must ensure the bandwidth is broad enough that the rise time will meet the spec. Write the expression for  $\frac{aB}{1+aB}$  in normalized form assuming  $a(s) = G_0 s$ . You will see that it is a quadratic low-pass filter. Find expressions for  $\omega_0$  and  $\zeta$  in terms of  $G_0$  and  $\tau = RC$ . For a second order circuit, tr (rise time) depends on both  $\omega_0$  and  $\zeta$ , however for a first order circuit with transfer function

$H(s) = \frac{1}{1+\frac{s}{\omega_0}}$ , the rise time can be calculated as  $t_r = 2.2\omega_0$ . In a second-order system, with

small  $\zeta$  values, the rise time will be shorter than this limit. Using this limit, what is the minimum

value of G (the unity gain bandwidth in Hz) needed for the circuit? Will the minimum G of the LF411 be satisfactory? Provide calculations. (Look up the datasheet for the min G value for the LF411 op-amp). The spec provided in the introduction part of the lab states the requirement on the rise time.

## Part 4)

Estimate  $\zeta$  using the typical value of G for the LF411. What overshoot would you expect? Use

$OS\% = 100 * e^{\sqrt{\frac{-\pi\zeta}{1-\zeta^2}}}$ . Clearly, this will not meet the spec. The problem is that the phase margin of the loop gain is rather small. We must increase the phase margin to at least  $45^\circ$ . Make a Bode plot of  $a(s)B(s)$  using MATLAB, find the unity gain frequency, and then read off the phase margin. Use the provided MATLAB script to find the phase margin.

## Part 5)

We can improve the phase margin by modifying the loop gain. Adding a zero near the unity gain frequency can be very helpful in such cases. You can do this by putting a compensation resistor  $R_C$  in series with the input C. Write the modified expression for  $a(s)B(s)$ . You will see that

adding  $R_C$  places a zero at  $\frac{1}{R_C C}$ . Find the value of  $R_C$  that puts this zero at the unity gain frequency. Create the Bode plots of the compensated loop gain,  $a(s)B_C(s)$ , and find the new phase margin. Show that you can obtain exactly the same effect by putting  $C_C$  in parallel with R instead of  $R_C$  in series with C. Create the Bode plots of the revised loop gain.

## Part 6)

We need to check the overshoot with the compensation resistor. The overshoot should be much smaller but may still be over the spec. Increase  $R_C$  until the overshoot just meets the spec. Check the phase margin with this  $R_C$ .

## Section 2: Circuit Level Spice Simulation

The system-level design was done using a rather simple model for the op-amp, and it may be too simple to get the behavior exactly correct. Thus, we must simulate the circuit using a macro model for the desired op-amp. (A macro model is a simplified circuit model that captures most (though not all) the circuit's behavior using a simplified schematic.)

### **Part 1)**

Simulate the original differentiator (with  $R_C = 0\Omega$ ) using the specified input triangle wave and the LF411 op-amp. Plot the input and output waveforms and measure the rise time and the overshoot. Include the simulation result in your report.

### **Part 2)**

Repeat the simulation with the calculated value of  $R_C$ . Measure the rise time and overshoot. Does it meet the spec? It should be close. If it does not meet the spec, adjust  $R_C$  until it does meet the spec. Include the simulation result in your report.

### **Part 3)**

Find the  $C_C$  that should put a zero in exactly the same place as  $R_C$  and simulate to confirm that the rise time and overshoot are the same.  $C_C$  is the capacitor in parallel with R, instead of having  $R_C$  in series with C in the differentiator circuit. Include the simulation result in your report

## Section 3: Measurement

It is essential to test real systems where stability is an issue because small variations in the circuit may be quite important. In this case, the real op-amp significantly differs from its spice model, which can impact stability. Furthermore, the actual circuit, as constructed on a breadboard, has significant “stray” capacitance at the circuit nodes, which can be important too. Before you start, check the calibration on your scope probes and adjust if necessary. Would you expect slew rate limiting to be a factor with this circuit?

### **Part 1)**

Set up and measure the original differentiator (with  $R_C = 0\Omega$ ) using the specified input triangle wave. Measure the rise time and the overshoot. Make a hard copy of the waveform and your measurements. Include these results and a picture of your circuit setup in your report.

### **Part 2)**

Repeat the test with the calculated value of  $R_C$ . Measure the rise time and overshoot. Does it meet the spec? It should be close. If it does not meet the spec, adjust  $R_C$  until it does meet the spec. Make a hard copy of the waveform and your measurements.

### **Part 3)**

Try the test with the equivalent value of  $C_C$  instead of  $R_C$  and see if the overshoot and rise time are the same in real life.

# Results

## Section 1: System Level Design

Part 1)


(a)

1) Calculate required 'C'

$$V_o(t) = -RC \frac{dV_i(t)}{dt}$$



$$\Delta V_i(t) = 1V_{pp}$$

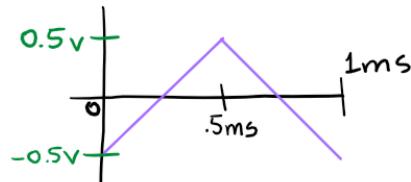

$$1 \text{ period} = T = \frac{1}{f} = \frac{1}{1 \text{ kHz}}$$

$$T = .001 \text{ s} = \underline{1 \text{ ms}}$$


$$V_o(t) = -RC \left[ \frac{-0.5 - 0.5}{0.0005(s)} \right]$$

$$(1V) = -(100K) \cdot C \cdot (-2000)$$

$$C = \frac{1}{200M} = 5 \times 10^{-9} \text{ F}$$

$$C = 5 \text{nF}$$

(b)

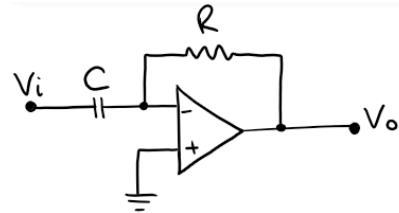

$$H(s) = \frac{\alpha B}{1 + \alpha B}, \quad \alpha(s) = \frac{G'}{s}, \quad B(s) = \frac{Z_I}{Z_I + Z_f}$$

$$H(s) = \frac{\left(\frac{G'}{s}\right) B}{1 + \left(\frac{G'}{s}\right) B} = \frac{G' B}{s(1 + \frac{G' B}{s})} \quad B(s) = \frac{Z_c}{Z_c + Z_R}$$

$$H(s) = \frac{G' B}{s + G' B} = \frac{\left(\frac{1}{sC}\right)}{\left(\frac{1}{sC}\right) + R} \cdot \left(\frac{sC}{sC}\right)$$

$$H(s) = \frac{1}{1 + \frac{s}{G' B}} \quad B(s) = \frac{1}{1 + sRC}$$

$$H(s) = \frac{1}{1 + \frac{s}{G'}(1 + sRC)}$$

$$H(s) = \frac{1}{1 + \frac{s}{G'} + \frac{s^2 RC}{G'}}$$

Comparing to General Form

$$H(s) = \frac{1}{1 + 2s\omega_0 + \frac{s^2}{\omega_0^2}}$$

Finding  $\omega_0$

$$\frac{1}{\omega_0^2} = \frac{R C}{G'}$$

$$\omega_0 = \sqrt{\frac{G'}{RC}} = \sqrt{\frac{G'}{\tau}}$$

Finding Zeta ( $\zeta$ )

$$\frac{2s}{\omega_0} = \frac{1}{G'}$$

$$\zeta = \frac{\omega_0}{2G'} = \frac{\left(\sqrt{\frac{G'}{\tau}}\right)}{G'}$$

$$\zeta = \frac{1}{2G'} \cdot \sqrt{\frac{G'}{\tau}}$$

$$= \sqrt{\frac{G'}{4(G')^2 \tau}}$$

$$\zeta = \sqrt{\frac{1}{4G'\tau}}$$

Finding minimum value of  $G'$

Rise time ( $t_r$ ) must be  $\leq 20\mu s$  (Given)

$$t_r = \frac{2.2}{\omega_0}$$

$$\therefore \frac{2.2}{\omega_0} \leq 20 \times 10^{-6}$$

$$\left( \frac{2.2}{\sqrt{\frac{G'}{\tau}}} \right) \leq 20 \times 10^{-6}$$

$$\frac{2.2}{20 \times 10^{-6}} \leq \sqrt{\frac{G'}{\tau}}$$

$$(1.21 \times 10^6) \leq \frac{G'}{\tau}$$

$$* \quad \tau = R C = (100k)(5nF) \quad *$$

$$\tau = 500\mu s$$

$$(1.21 \times 10^6) (500 \times 10^{-6}) \leq G'$$

$$6.05 \times 10^6 \left( \frac{\text{rad}}{\text{s}} \right) \leq G'$$

\* unit conversion \*

$$\frac{\text{rad}}{\text{s}} \rightarrow \text{Hz} \quad (\frac{1}{s})$$

$$\frac{G'}{2\pi}$$

$$9.63 \times 10^5 \text{ Hz} \leq G'$$

The minimum  $G'$  of the LF 411 op-amp

must be greater than the calculated  $G'$

Which it satisfies

$$G'_{(\text{op-amp})} = 3 \times 10^6 > 9.63 \times 10^5$$

(c)

1c) Find expected overshoot

$$OS\% = e^{\frac{-\pi \zeta}{\sqrt{1-\zeta^2}}}$$

$$\zeta = \sqrt{\frac{1}{4G\tau}} = \sqrt{\frac{1}{4(3 \times 10^6)(500 \times 10^{-6})}}$$

$$\zeta = 0.01291$$

$$OS\% = \left( e^{\frac{-\pi(0.01291)}{\sqrt{1-(0.01291)^2}}} \right) \times 100$$

$$OS\% = e^{-0.04056} \times 100$$

$$OS\% = 96.03\%$$

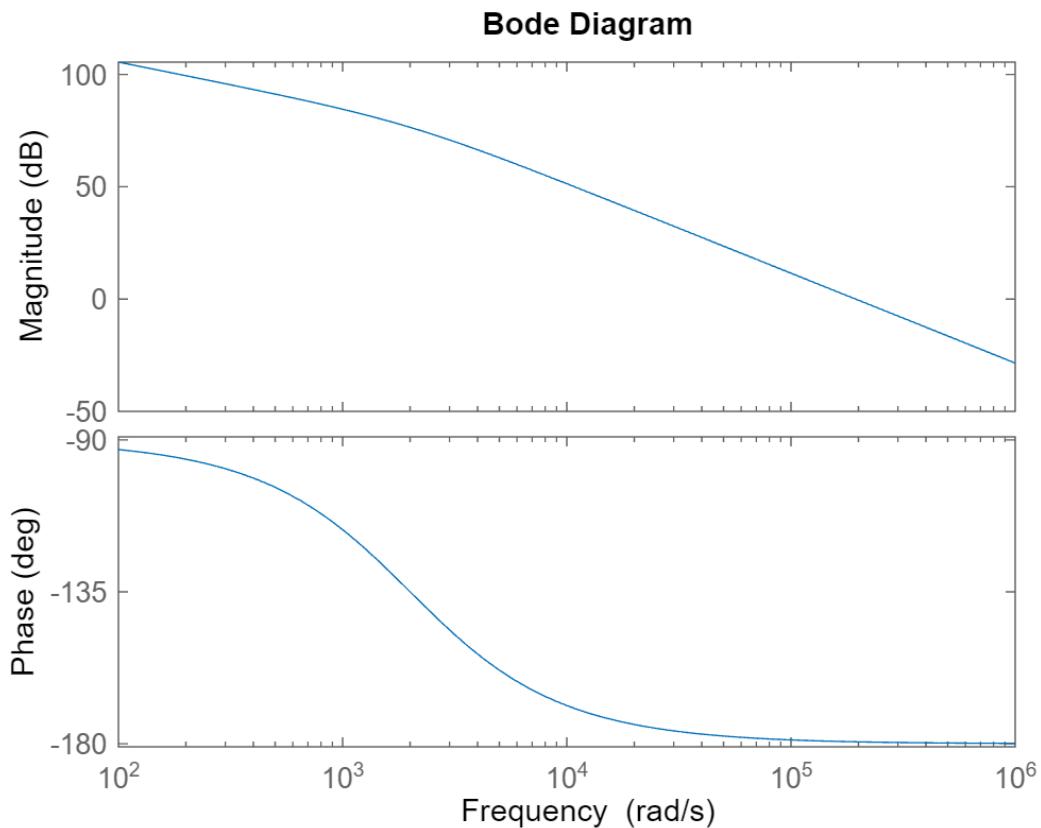


Figure 1.3.1: Bode Plot of Circuit without Compensation

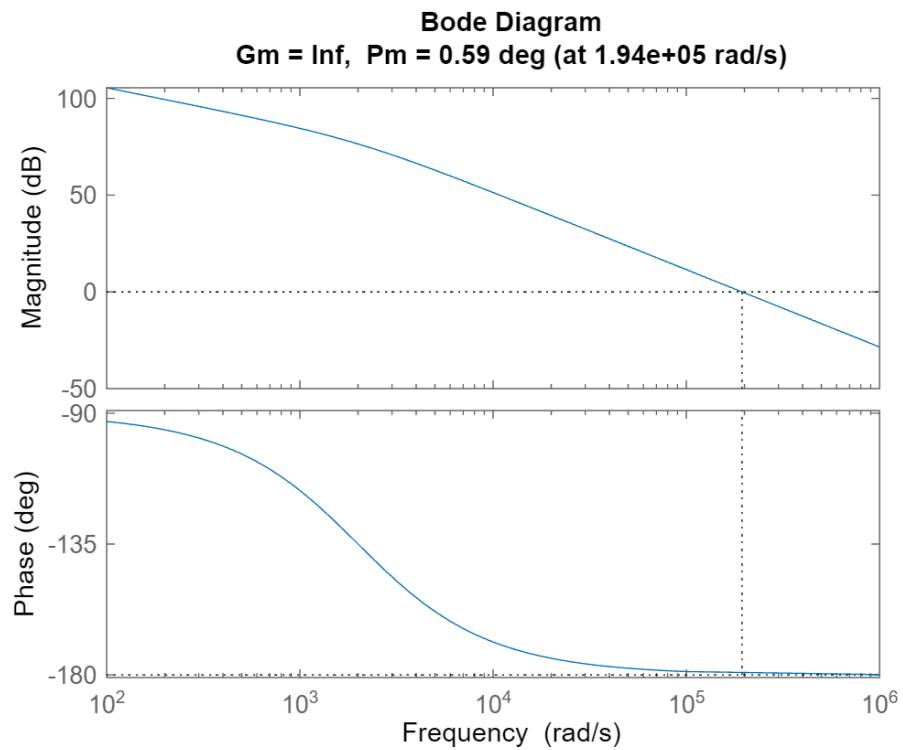


Figure 1.3.2: Bode Plot


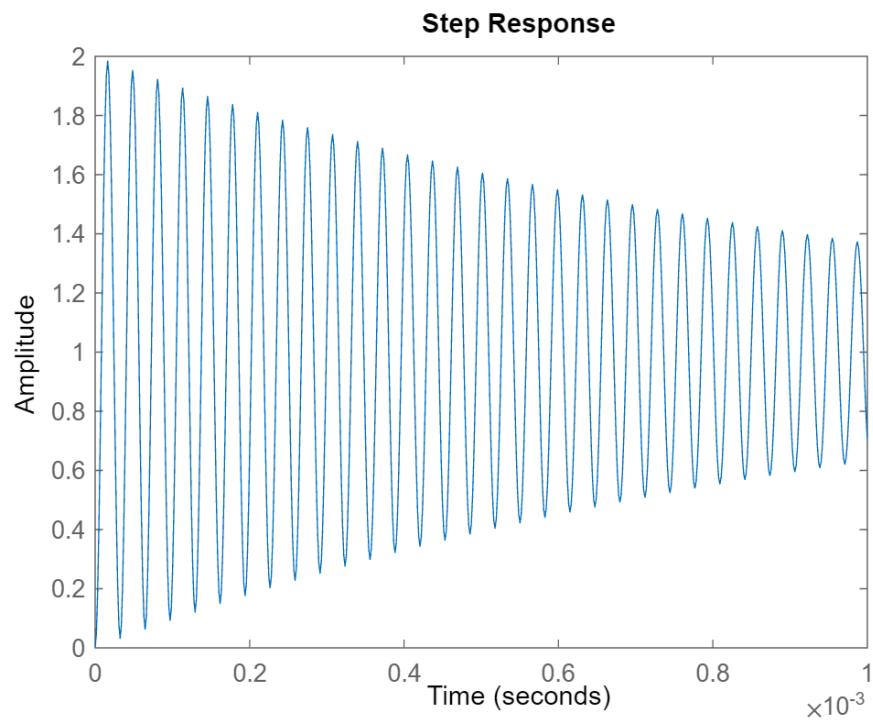


Figure 1.3.3: Step Response of Circuit without Compensation

(d)

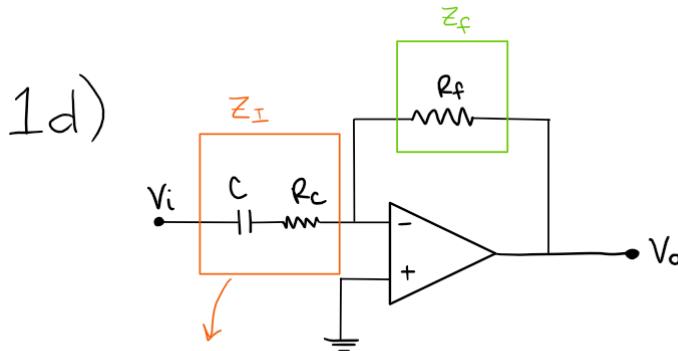In order to minimize the amount of overshoot, we place a Compensation Resistor in series with the input capacitor.



$$Z_I = \frac{1}{sc} + R_c = \frac{1 + sR_c C}{sc}$$

$$B(s) = \frac{Z_I}{Z_I + Z_f} = \frac{\left(\frac{1 + sR_c C}{sc}\right)}{\left(\frac{1 + sR_c C}{sc}\right) + R_f}$$

$$= \frac{\left(\frac{1 + sR_c C}{sc}\right)}{\left(\frac{1 + sR_c C + sR_f C}{sc}\right)}$$

$$B(s) = \frac{1 + sR_c C}{1 + sc(R_c + R_f)} \quad (1)$$

Find value of  $R_c$  that makes  
 $B(s) = 0$

$$1 + sR_c C = 0$$

$$R_c = \frac{-1}{sc}$$

$$|s| = \left| \frac{-1}{R_c C} \right|$$

$$R_c = \frac{1}{sc}$$

$$R_c = \frac{1}{(1.94 \times 10^5)(5 \times 10^{-9})}$$

$$R_c = 1.03 \text{ k}\Omega$$

*s = calculated from MATLAB*

$$|s| = 1.94 \times 10^5 \frac{\text{rad}}{\text{s}}$$

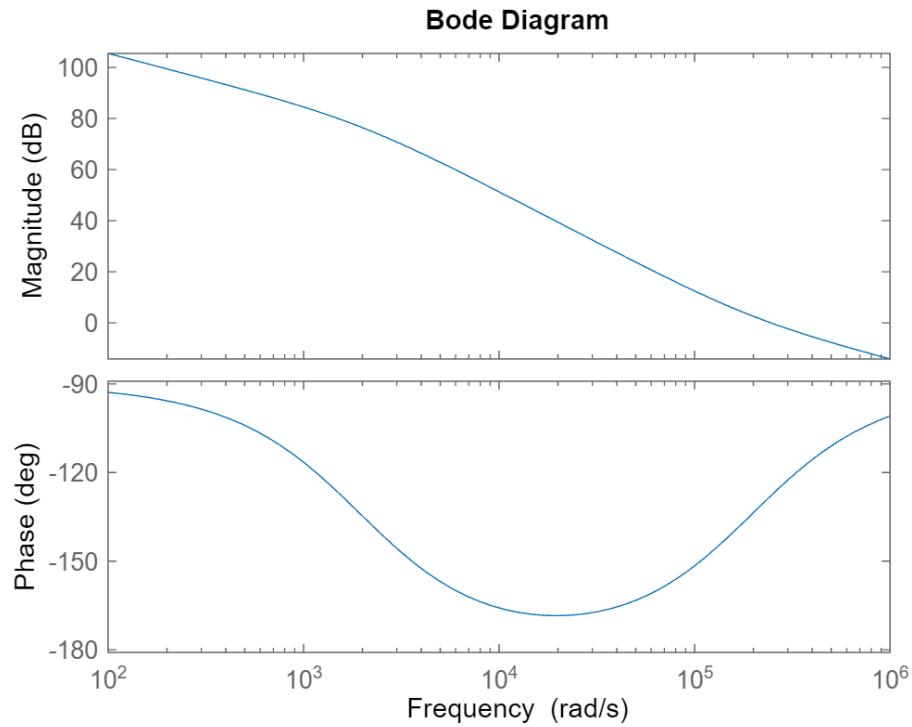


Figure 1.4.1: Bode Plot of Circuit with Compensation Resistor

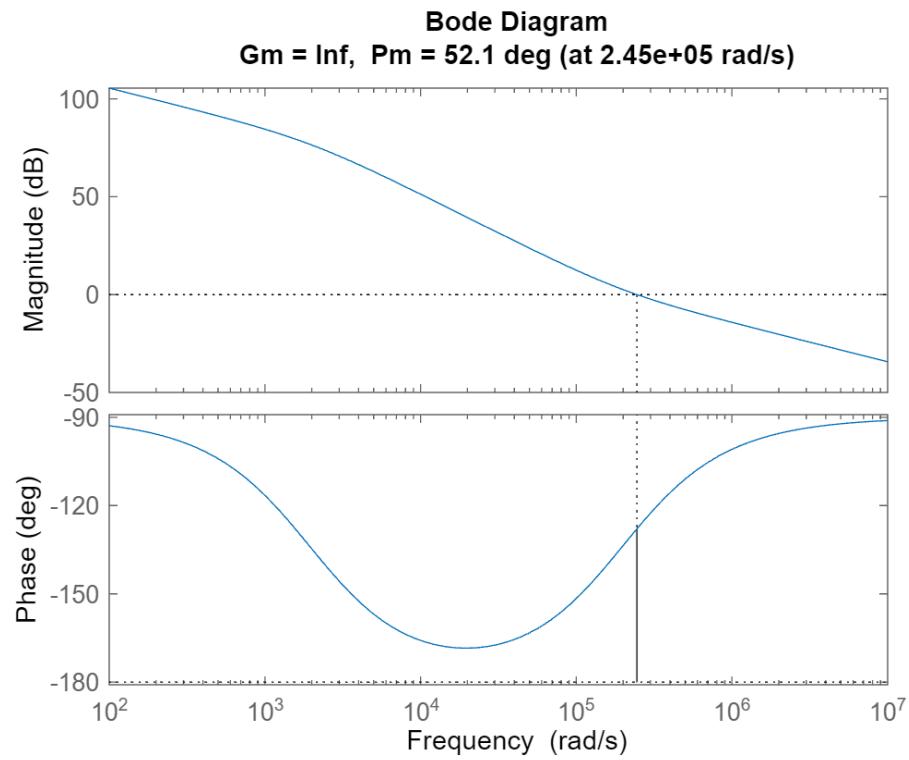


Figure 1.4.2:

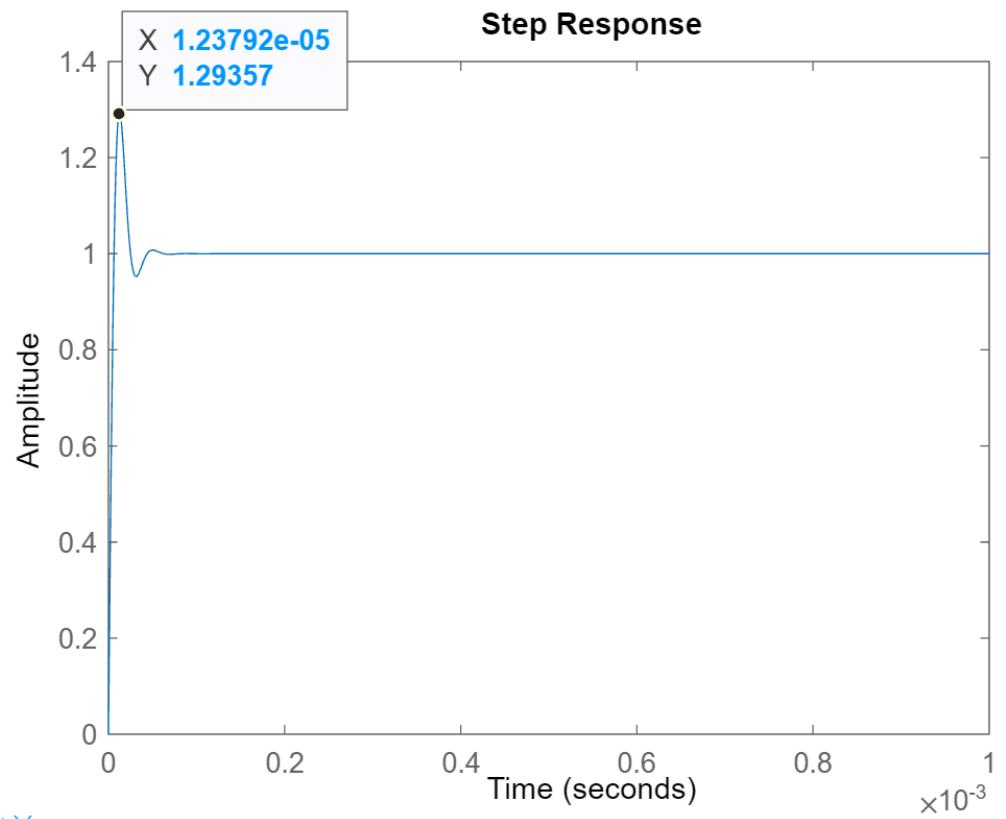


Figure 1.4.3: Step Response of Circuit with Compensation Resistor

Now we place a Compensation Capacitor in parallel with the feedback resistor and repeat the process. In the end we should get the same effects, proving the circuits function equivalently.

The circuit diagram shows a non-inverting op-amp configuration. The input voltage  $V_i$  is applied through a voltage divider consisting of a capacitor  $C$  and a resistor  $Z_I$ . The output of the voltage divider is connected to the non-inverting input of the op-amp. The inverting input is grounded. A feedback path is formed by the op-amp's output  $V_o$ , a resistor  $R_f$ , and a compensation capacitor  $C_c$  connected in parallel with  $R_f$ . A green box highlights the parallel combination of  $C_c$  and  $R_f$ , labeled  $Z_f$ .

$$Z_f = \frac{(R_f)(\frac{1}{sc})}{R_f + \frac{1}{sc}}$$

$$= \frac{\frac{R_f}{sc}}{1 + scR_f}$$

$$B(s) = \frac{Z_I}{Z_I + Z_f} = \frac{\frac{1}{sc}}{\left(\frac{1}{sc} + \frac{R_f}{1 + scR_f}\right)} \cdot \frac{scC_c}{scC_c}$$

$$= \frac{1}{1 + \frac{scR_f}{1 + scR_f}}$$

$$= \frac{1}{\left(\frac{1 + scR_f + scR_f}{1 + scR_f}\right)}$$

$$B(s) = \frac{1 + sc_c R_f}{1 + sR_f(C + C_c)}$$

Finding value of  $C_c$  that makes  $B(s)=0$

$$1 + sc_c R_f = 0$$

$$|s| = \left| \frac{-1}{C_c R_f} \right|$$

$$1.94 \times 10^5 = \frac{1}{C_c R_f}$$

$$C_c = \frac{1}{(1.94 \times 10^5)(100K)}$$

$$C_c = 5.155 \times 10^{-11} F$$

$$C_c = 51.55 \mu F$$

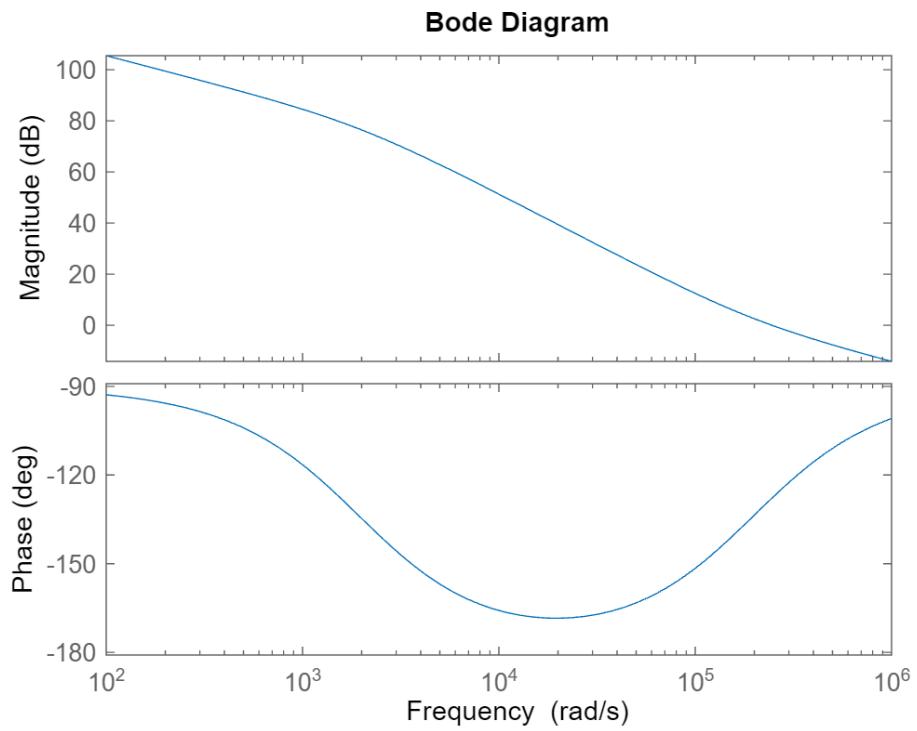


Figure 1.4.4: Bode Plot of Circuit with Compensation Capacitor

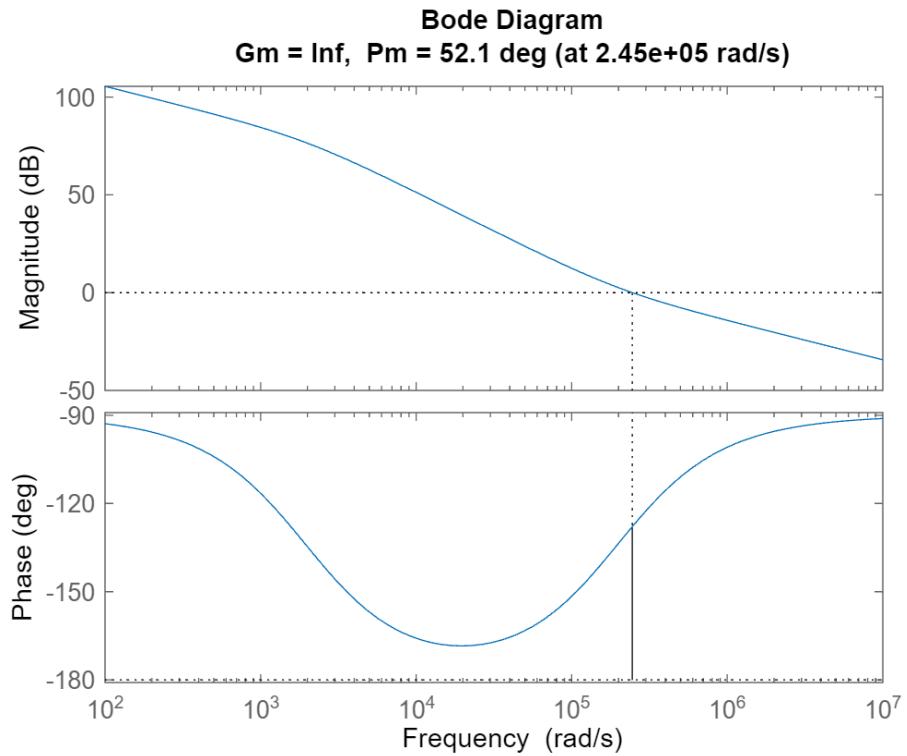


Figure 1.4.5: n Resistor

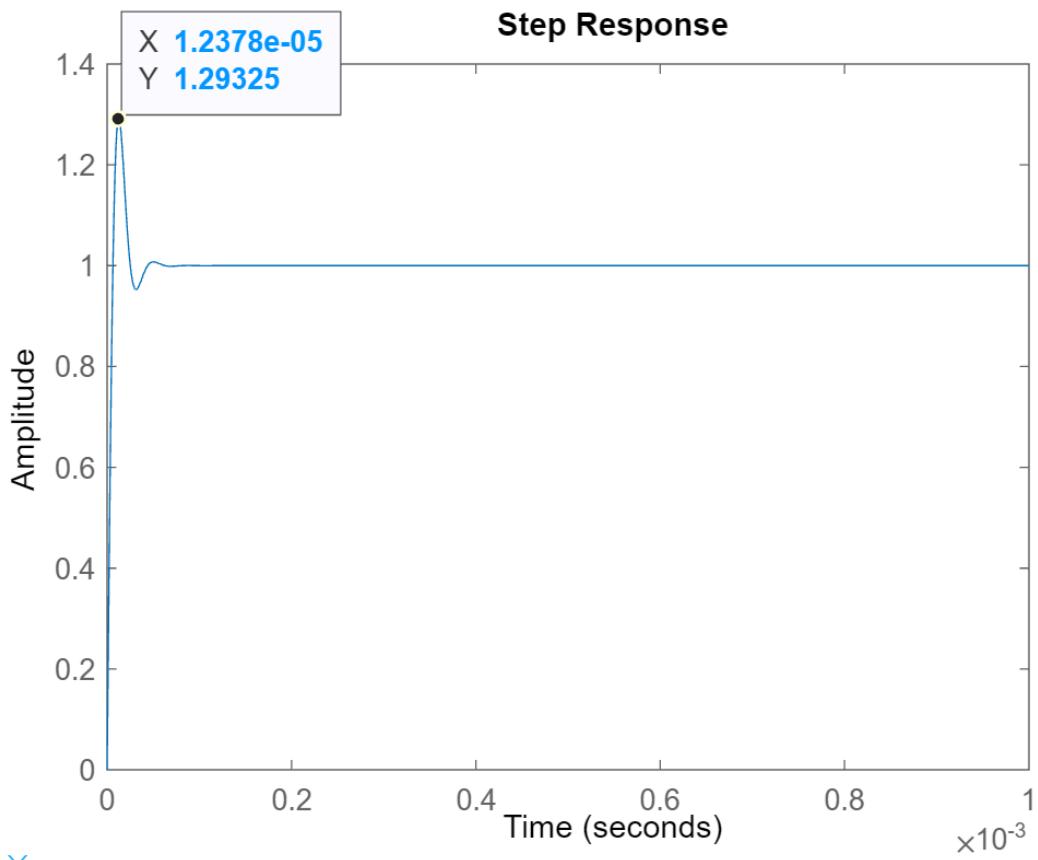


Figure 1.4.6: Step Response of Circuit with Compensation Capacitor

(e)

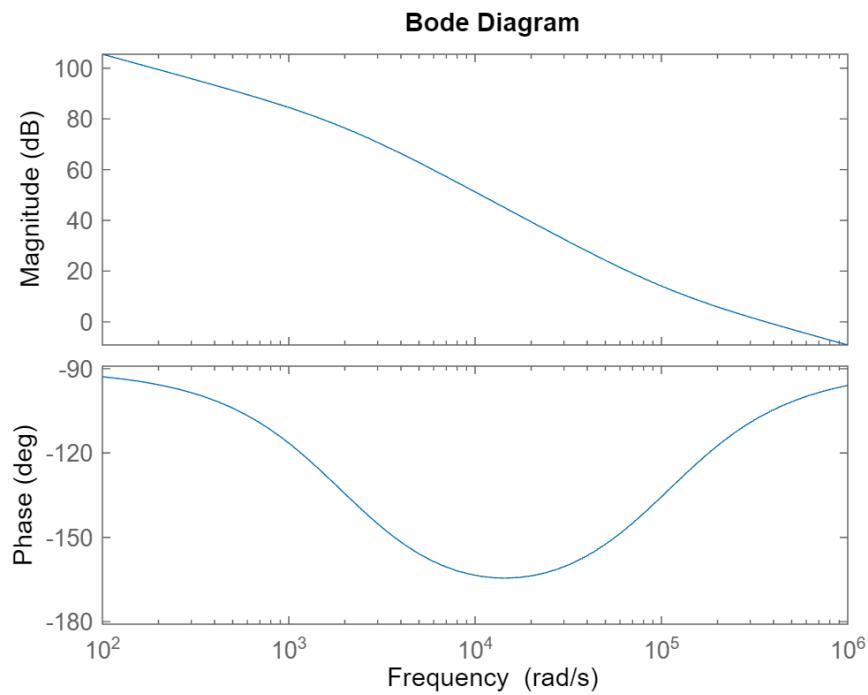


Figure 1.5.1:

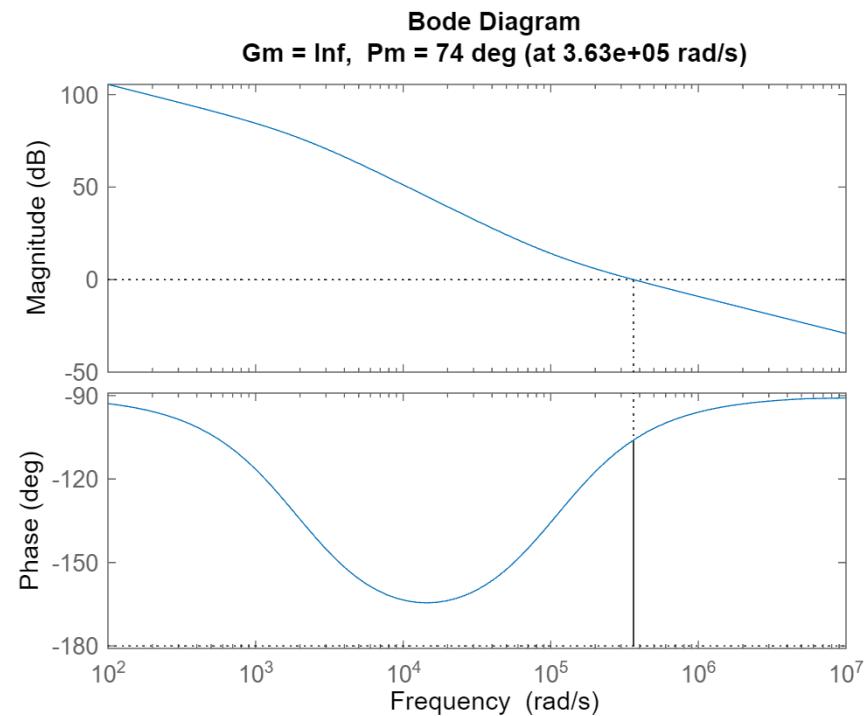


Figure 1.5.2:

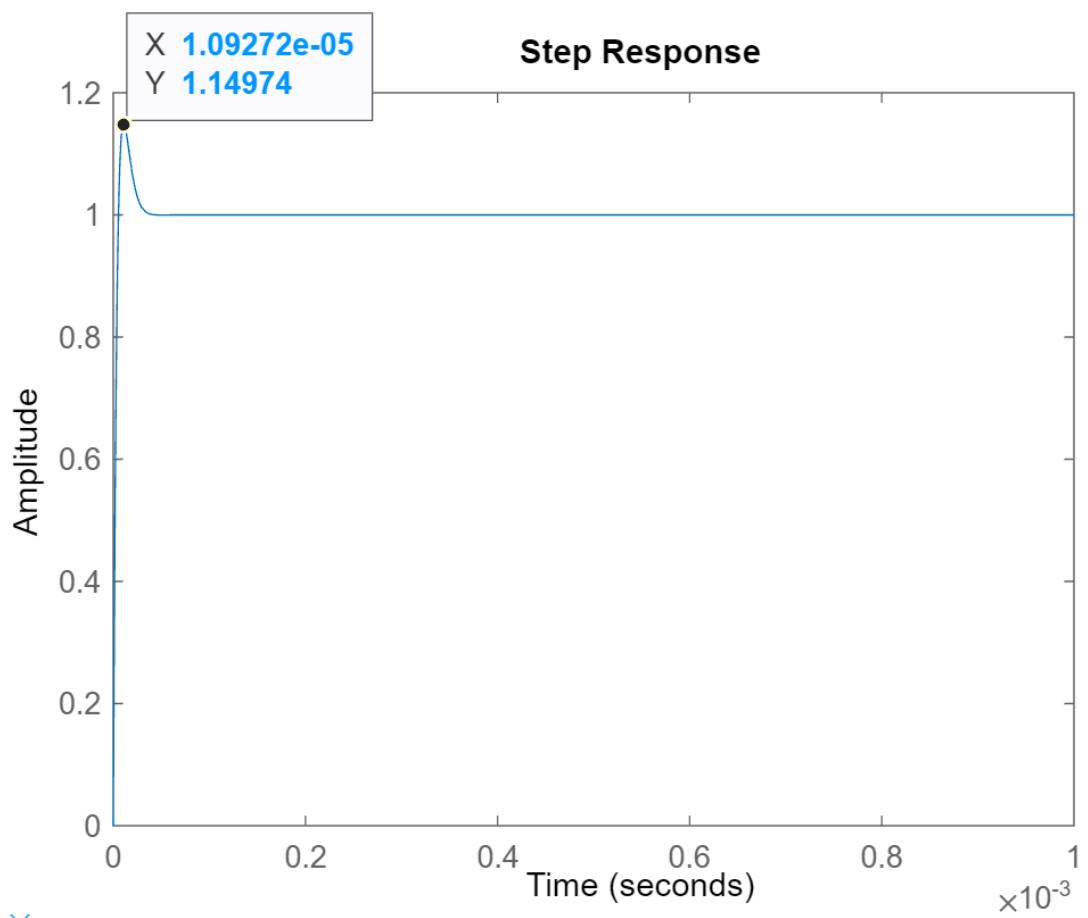


Figure 1.5.3:

## Section 2: Circuit Level Spice Simulation

The goal is to simulate and compare the rise time and the amount of overshoot with varying Compensation Components. To do this we must perform calculations. Our requirement for overshoot is that it must be **no greater than 15%** in order for the circuit to be considered properly compensated.

### Calculating Overshoot

$$\text{Overshoot \%} = \left( \frac{V_o^{\text{Max}} - V_2}{V_2 - V_1} \right) \times 100$$

$$\text{Overshoot \%} = \left( \frac{2.64 - 1}{1 - (-1)} \right) \times 100$$

$V_1$  = Upper Steady State Voltage

$V_2$  = Lower Steady State Voltage

### Calculating Rise Time

$$V_x = V_1 + 10\% * (V_2 - V_1)$$

$$V_y = V_1 + 90\% * (V_2 - V_1)$$

$$\text{Rise Time } (t_r) = t_2 - t_1$$

## Part 1)

As a control we simulated the circuit using an Ideal Op-Amp to compare to our actual circuit.

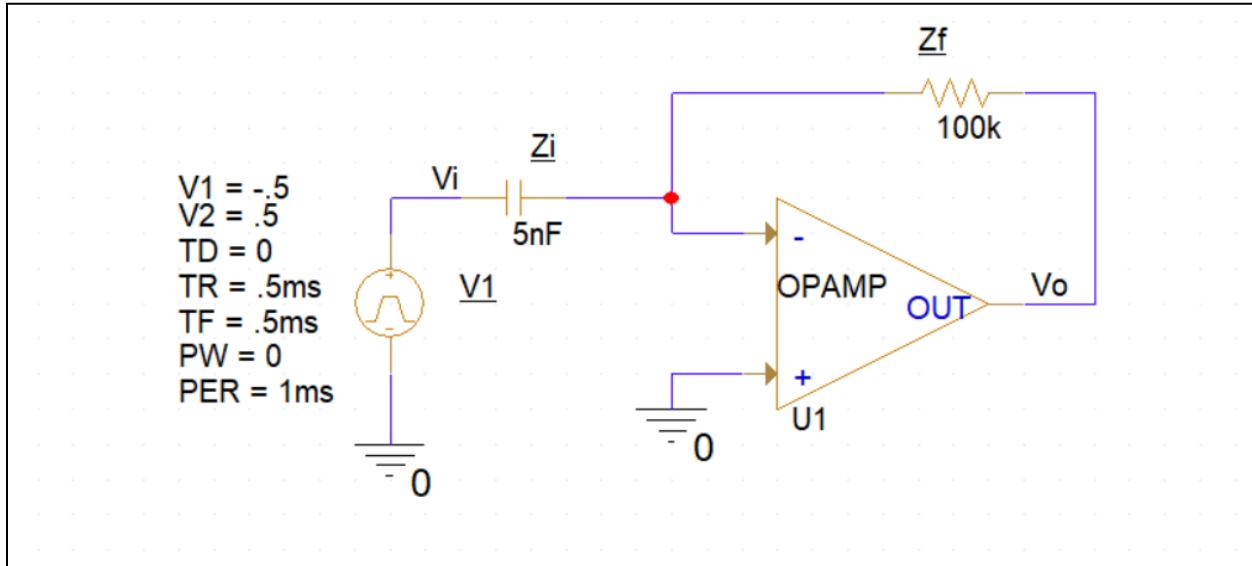


Figure 2.1.1: Schematic of Ideal Differentiator Circuit Macro Model

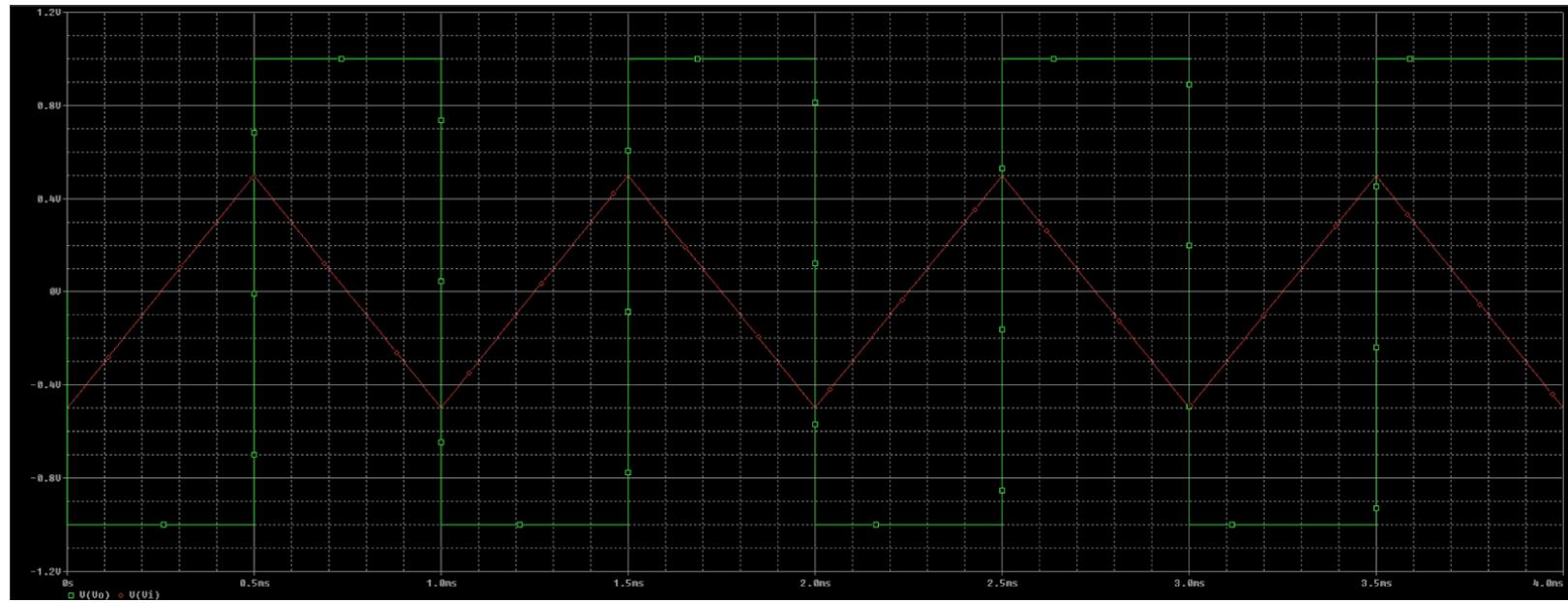


Figure 2.1.2: Simulation Plot of Ideal Differentiator Macro Model

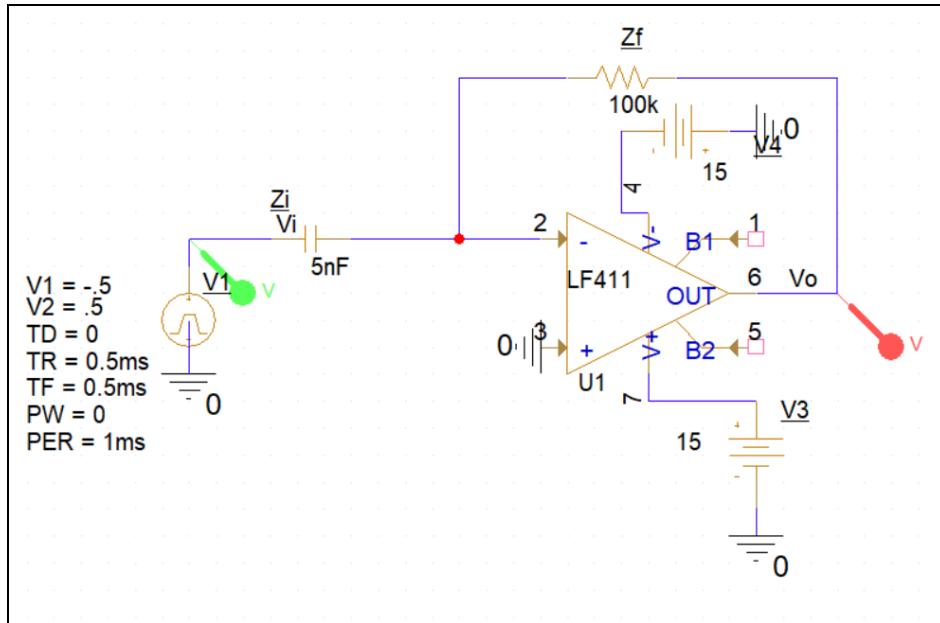


Figure 2.1.3: Schematic of Differentiator Circuit with LF411

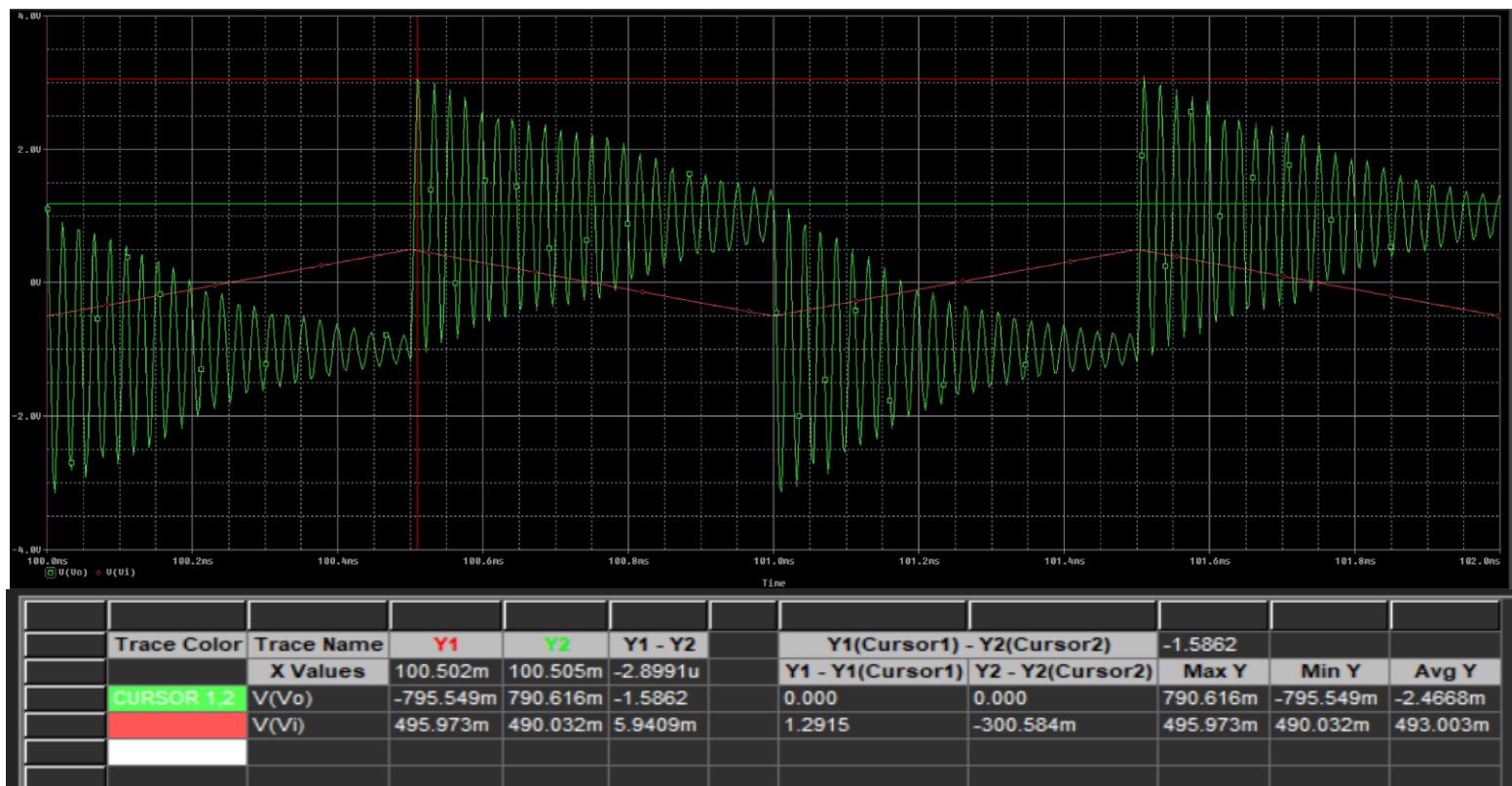


Figure 2.1.4: Simulation Plot and Trace of Differentiator with LF411

Rise Time:  $-2.8991\mu\text{s}$

## Part 2)

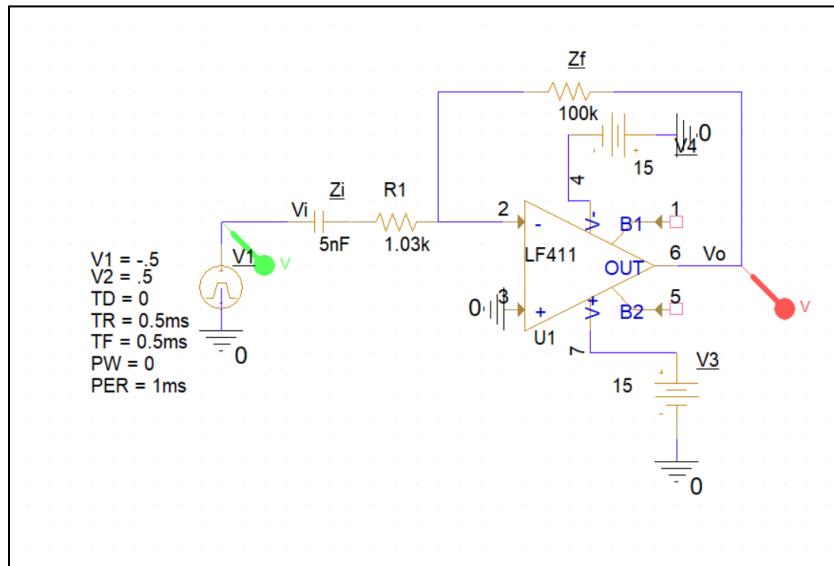


Figure 2.2.1: Schematic of Differentiator Circuit with  $R_C = 1.03K\Omega$

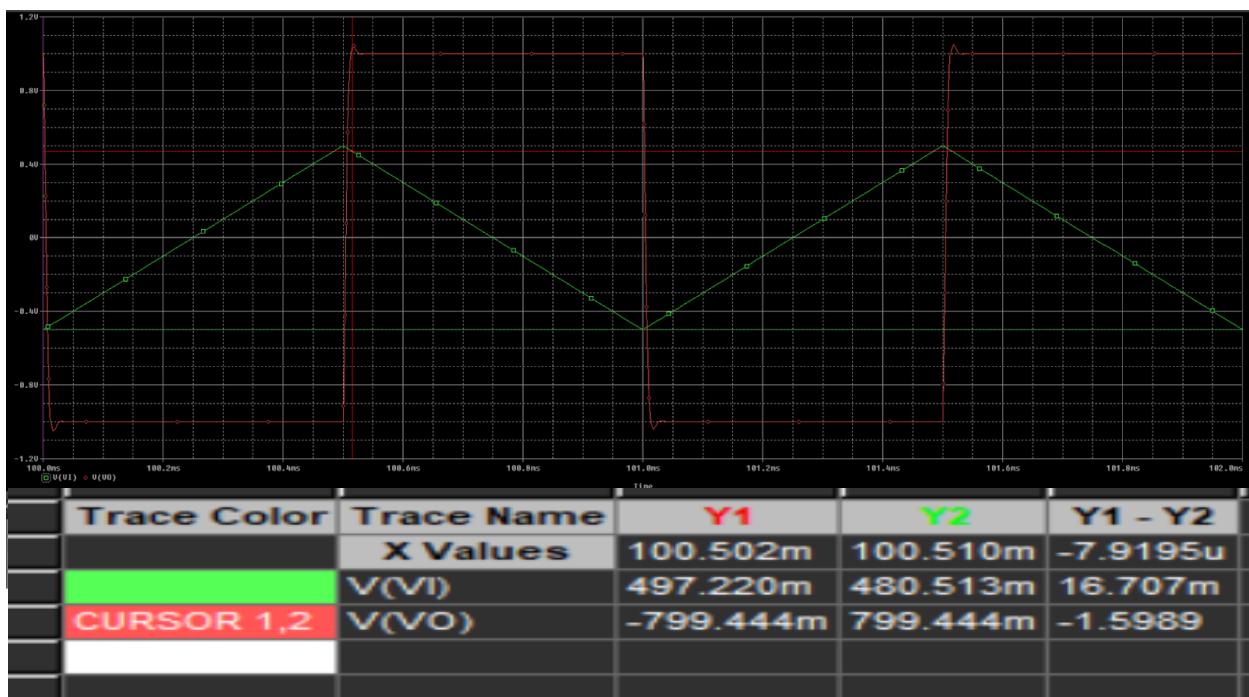


Figure 2.2.2: Simulation Plot and Trace with  $R_C = 1.03K\Omega$

$$\text{Overshoot \%} = \left( \frac{1.0465 - 1}{1 - (-1)} \right) \times 100 = 2.3\%$$

Rise Time:  $-7.9195\mu\text{s}$

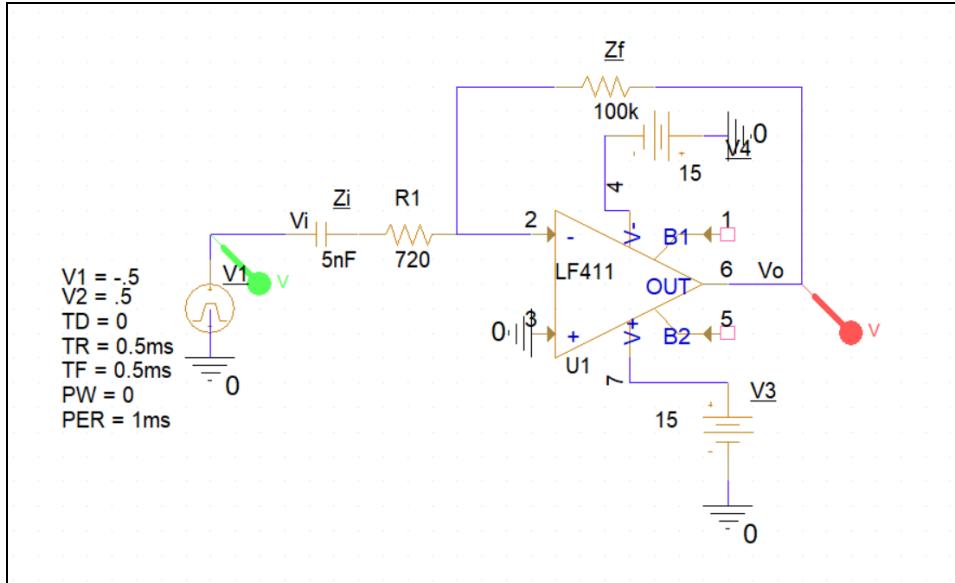


Figure 2.2.3: Schematic of Differentiator Circuit with  $R_C = 720\Omega$

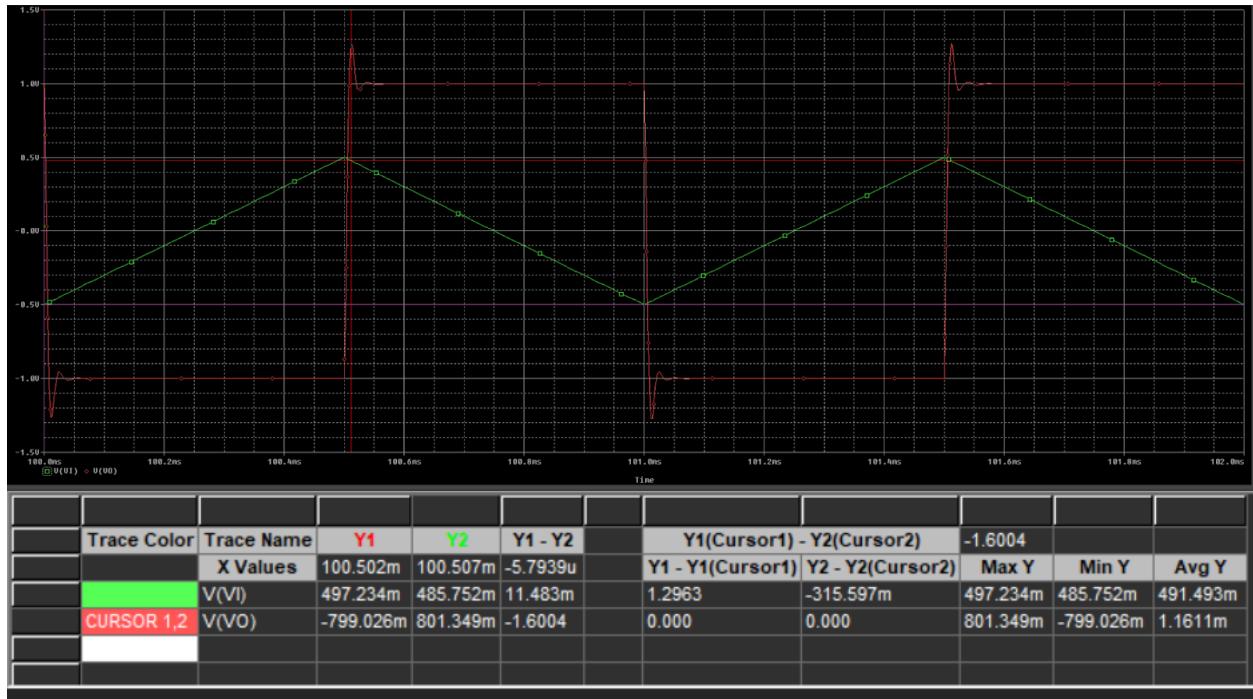


Figure 2.2.4: Simulation Plot and Trace with  $R_C = 720\Omega$

$$Overshoot \% = \left( \frac{1.2686 - 1}{1 - (-1)} \right) \times 100 = \mathbf{13.4\%}$$

Rise Time:  $\mathbf{-5.7939\mu s}$

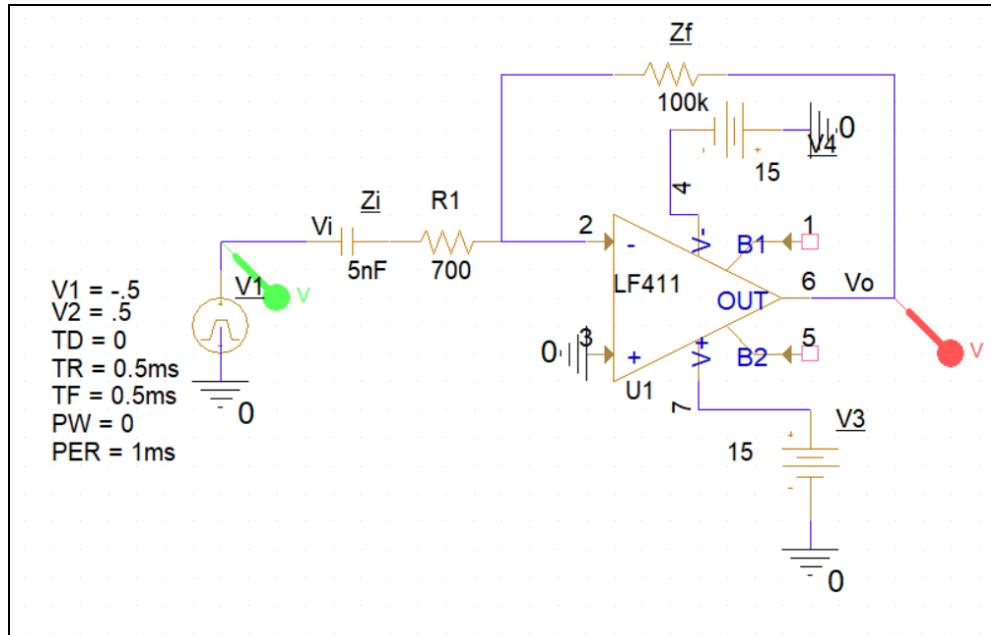


Figure 2.2.5: Schematic of Differentiator Circuit with  $R_c = 700\Omega$

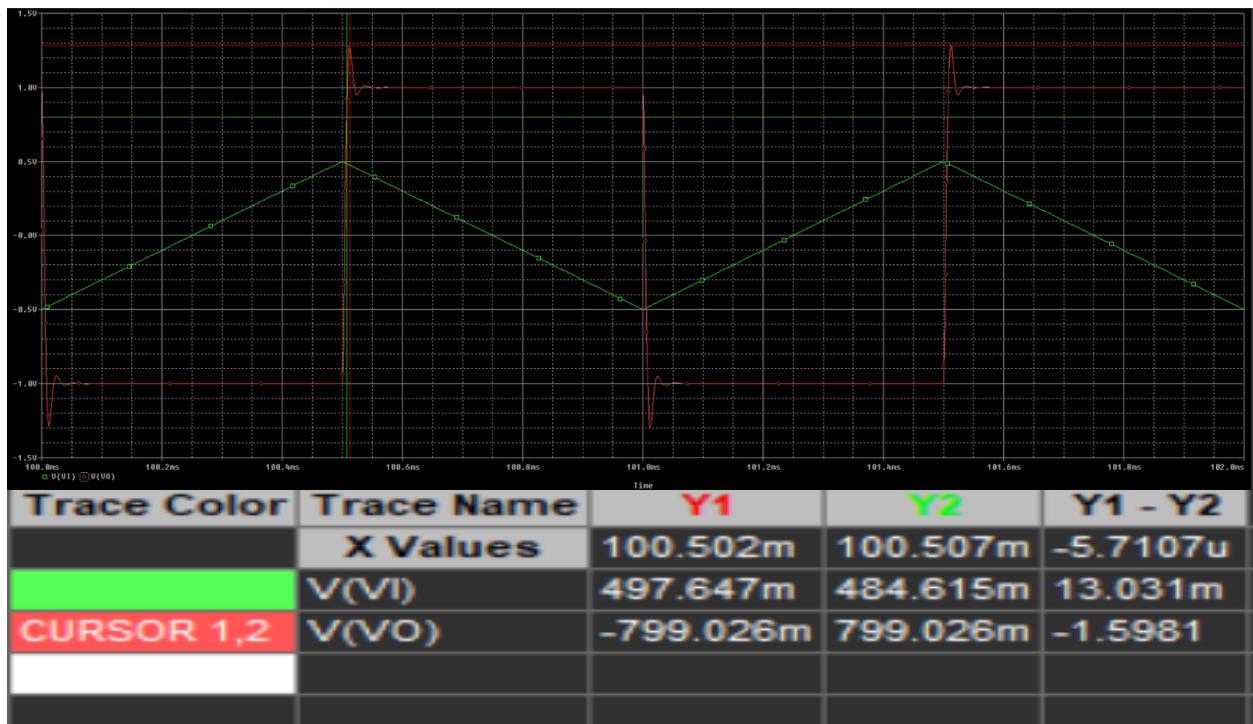


Figure 2.2.6: Simulation Plot and Trace with  $R_c = 700\Omega$

$$Overshoot \% = \left( \frac{1.2830 - 1}{1 - (-1)} \right) \times 100 = 14.2\%$$

Rise Time:  $5.7107\mu\text{s}$

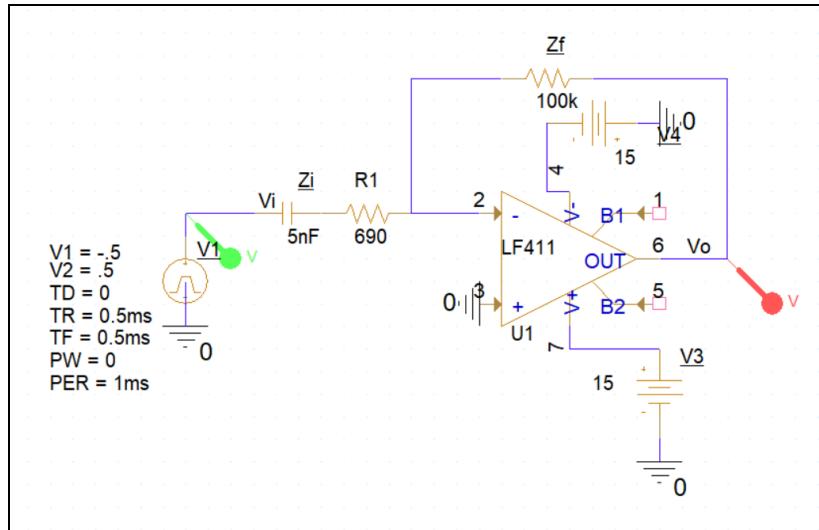


Figure 2.2.7: Schematic of Differentiator Circuit with  $R_C = 690\Omega$

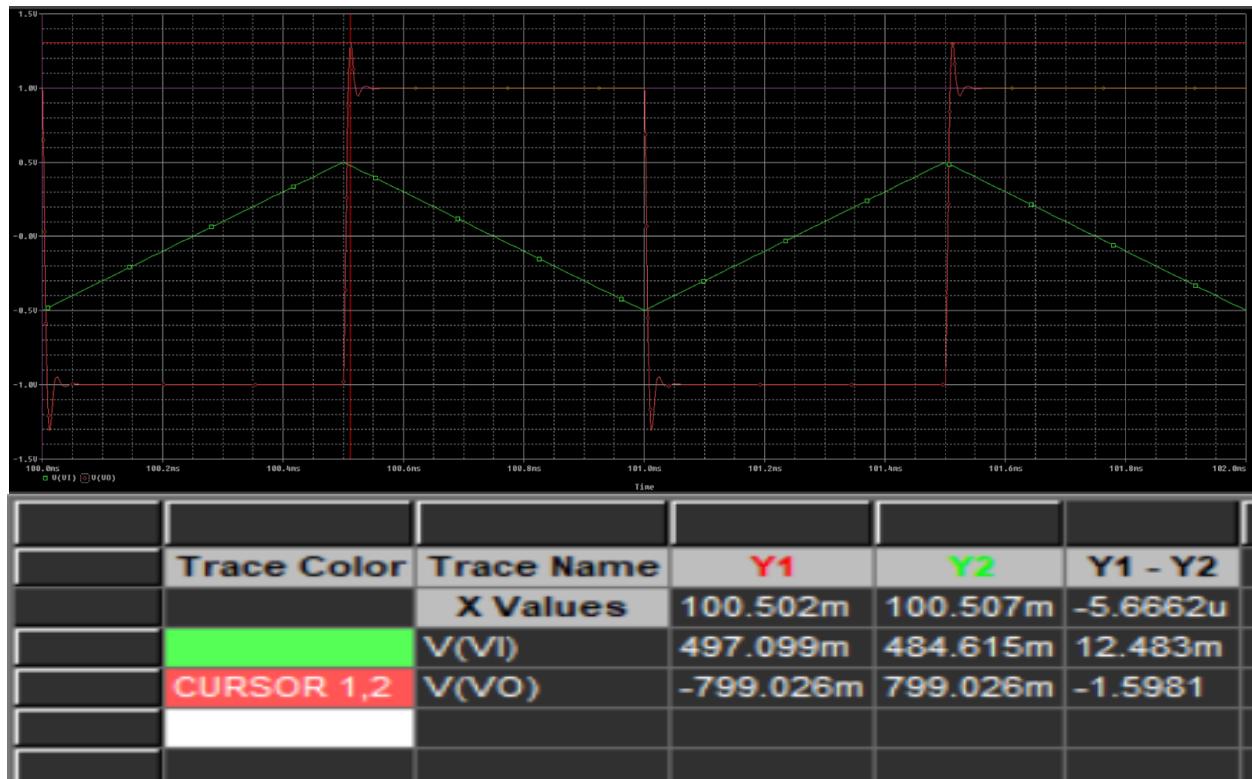


Figure 2.2.8: Simulation Plot and Trace with  $R_C = 690\Omega$

$$Overshoot \% = \left( \frac{1.3081 - 1}{1 - (-1)} \right) \times 100 = 15.4\%$$

Too much Overshoot

Rise Time:  $5.662\mu\text{s}$

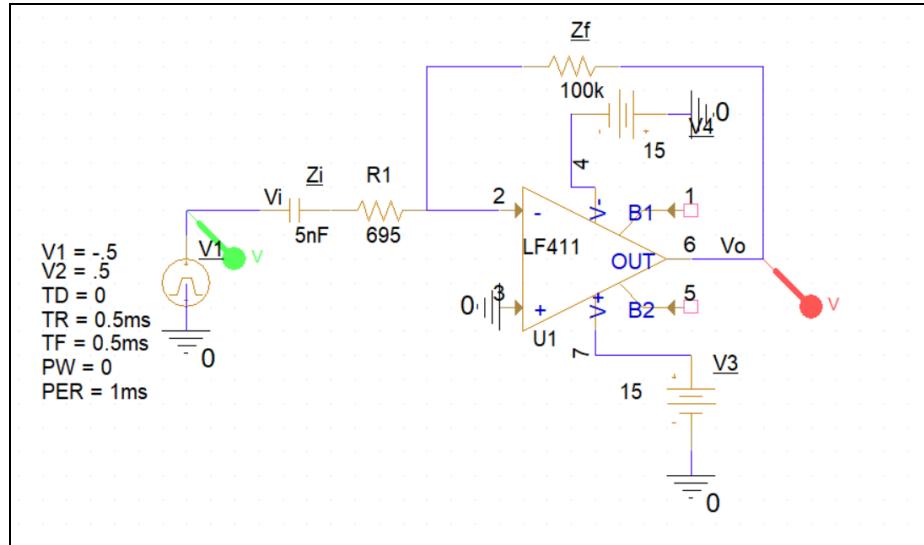


Figure 2.2.9: Schematic of Differentiator Circuit with  $R_C = 695\Omega$

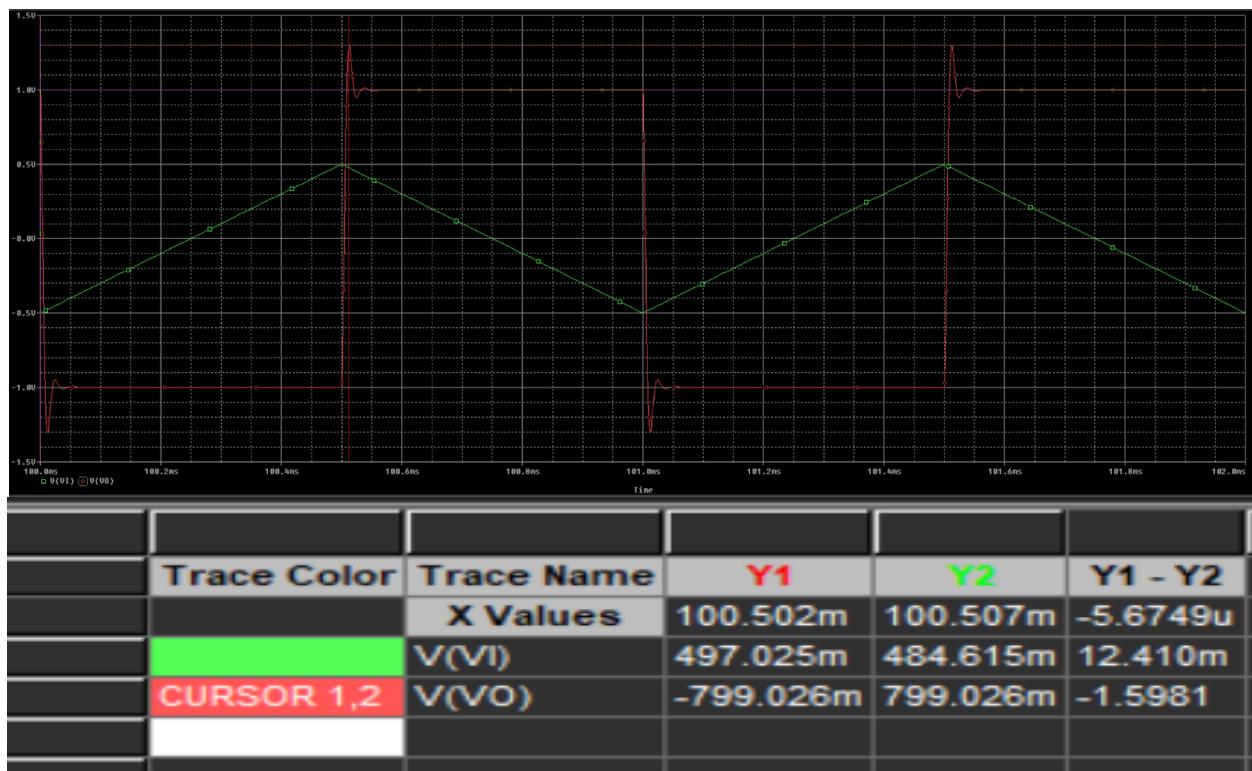


Figure 2.2.10: Simulation Plot and Trace with  $R_C = 695\Omega$

$$\text{Overshoot \%} = \left( \frac{1.2997 - 1}{1 - (-1)} \right) \times 100 = \mathbf{14.985\%}$$

Barely Meets the Spec

Rise Time = **5.6749us**

$R_c$ Value ( $\Omega$ )	Overshoot (%)	Rise Time ( $\mu\text{s}$ )
1.03k	2.3%	7.9195
720	13.4	5.7939
700	14.2 %	5.7107
690	15.4%	5.6620
695	14.985%	5.6749

Figure 2.2.11: Table of Simulated  $R_c$  Values

### Part 3)

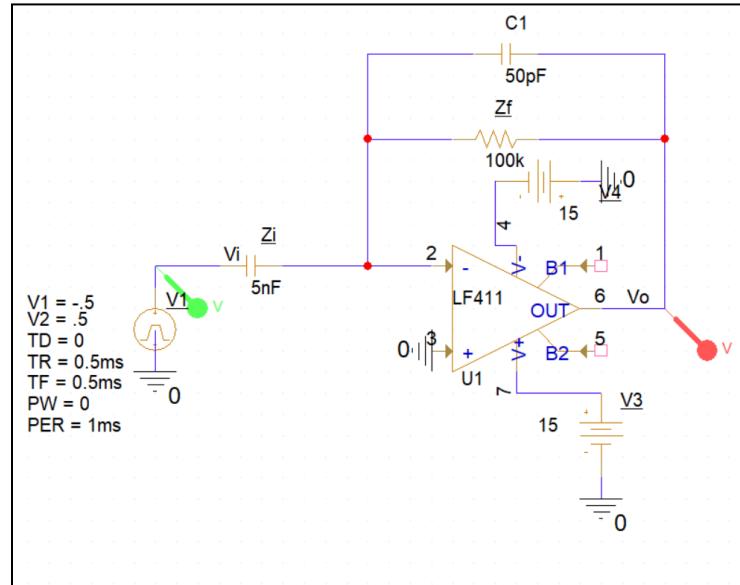


Figure 2.3.1: Schematic of Differentiator Circuit with  $C_c = 50\text{pF}$



Figure 2.3.2: Simulation Plot and Trace with  $C_c = 50\text{pF}$

$$\text{Overshoot \%} = \left( \frac{1.0631 - 1}{1 - (-1)} \right) \times 100 = 3.155\%$$

Rise Time:  $7.467\mu\text{s}$

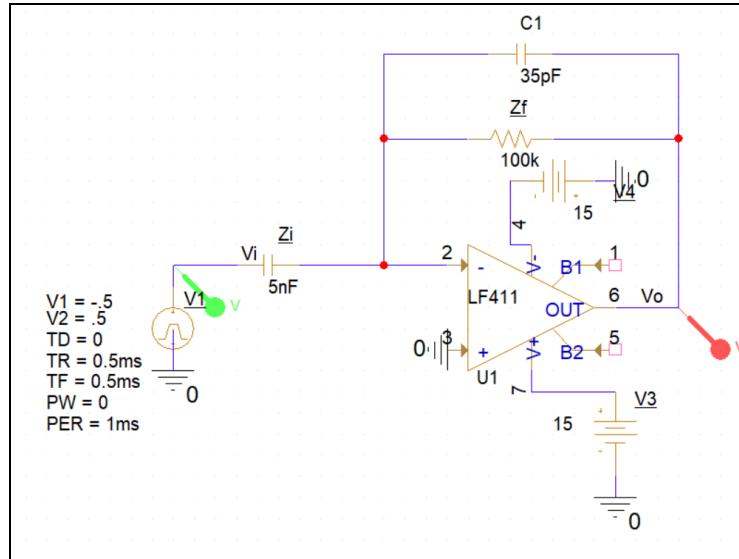


Figure 2.3.3: Schematic of Differentiator Circuit with  $C_c = 35\text{pF}$



Figure 2.3.4: Simulation Plot and Trace with  $C_c = 35\text{pF}$

$$\text{Overshoot \%} = \left( \frac{1.2872 - 1}{1 - (-1)} \right) \times 100 = \mathbf{14.360\%}$$

Rise Time:  $5.6765\mu\text{s}$

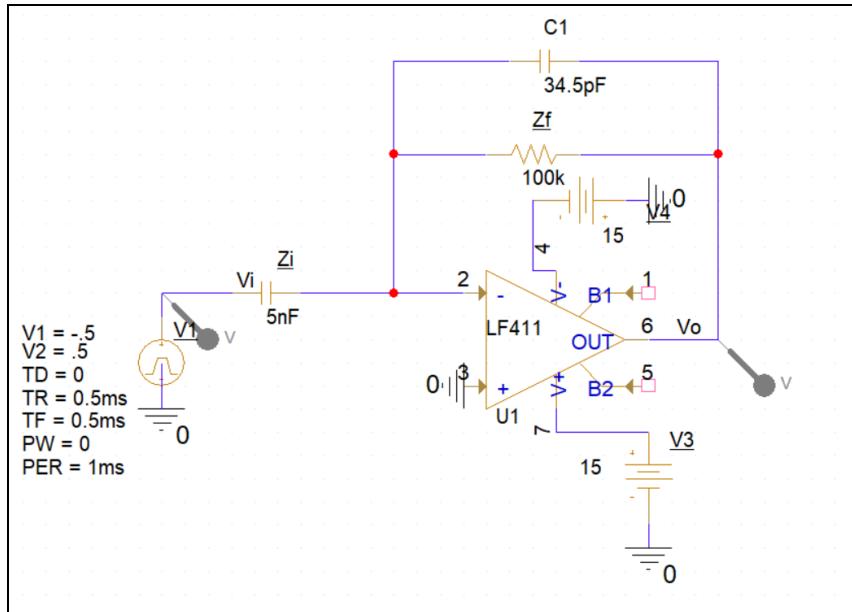


Figure 2.3.5: Schematic of Differentiator Circuit with  $C_c = 34.5\text{pF}$

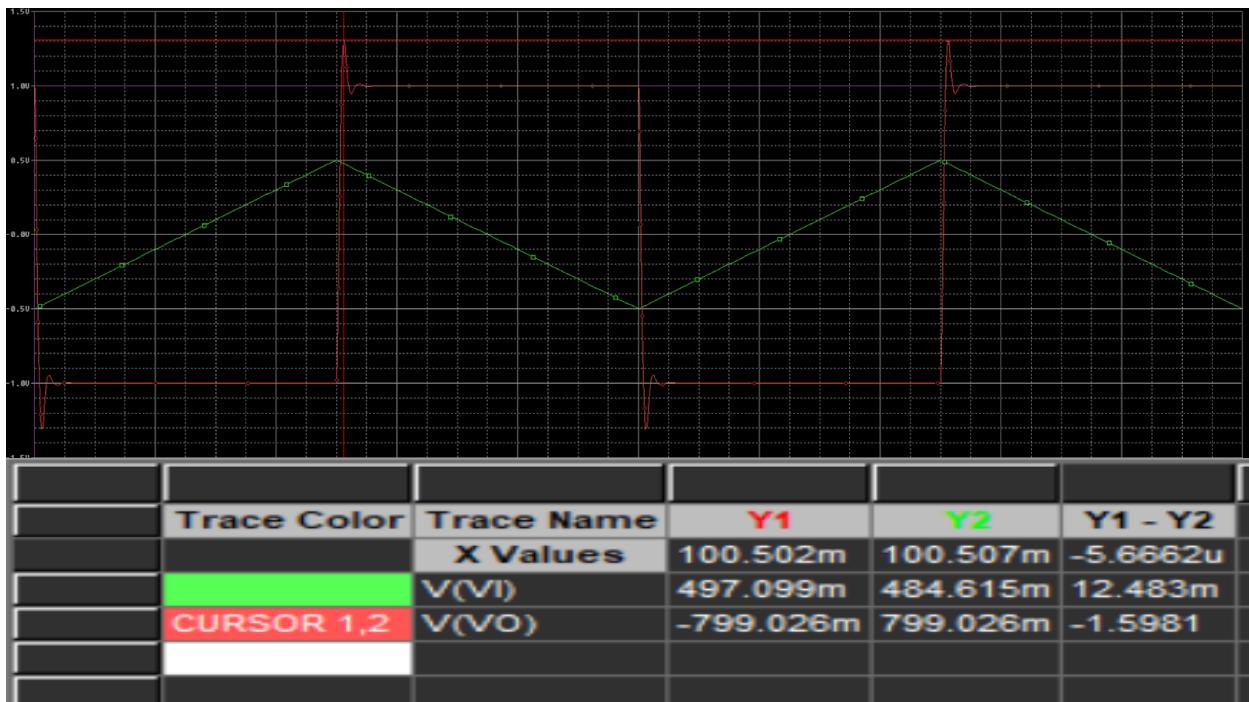


Figure 2.3.6: Simulation Plot and Trace with  $C_c = 34.5\text{pF}$

$$\text{Overshoot \%} = \left( \frac{1.3081 - 1}{1 - (-1)} \right) \times 100 = \mathbf{15.4\%}$$

Does not meet spec so 35pF is our final answer.

$C_c$ Value (pF)	Overshoot (%)	Rise Time (μs)
50	3.155	7.467
35	14.360	5.6765
34.5	15.4	5.5735

Figure 2.3.7: Table of Simulated Cc Values

## Section 3: Measurements

The LF411 has a slew rate of  $13V/\mu s$ , which is well beyond the requirements of our design, where the peak rate is only  $2.6V$  over  $20\mu s$ , equivalent to  $0.13V/\mu s$ . Therefore, the LF411's performance will not be a limiting factor in this context.

### Part 1)

For the first circuit we will measure the output without compensation to view the behavior.

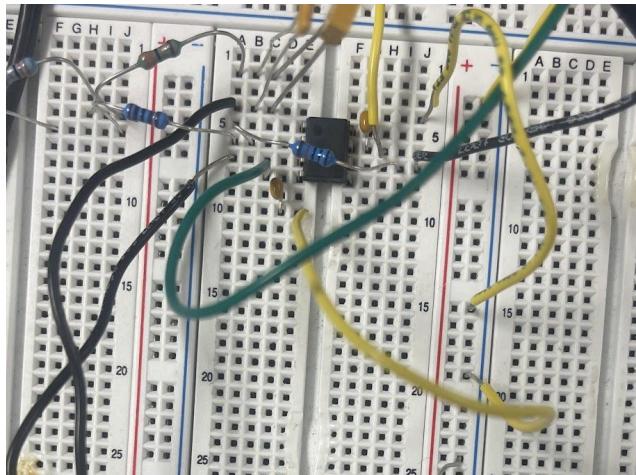


Figure 3.1.1: Breadboard Circuit without Compensation

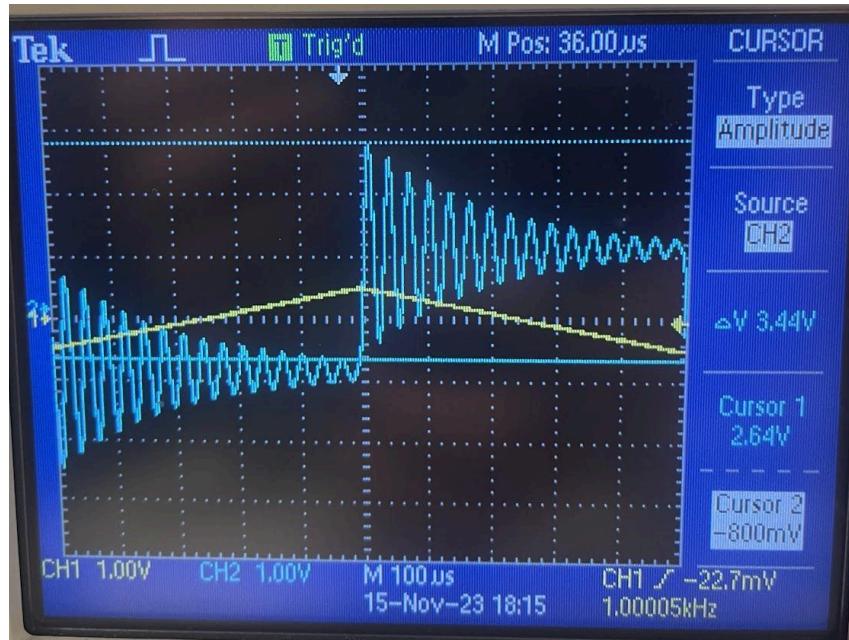


Figure 3.1.2: Oscilloscope Measurements without Compensation

$V_{out}$  (Blue) and  $V_{in}$  (Yellow)

## Part 2)

For the second circuit, we will use our simulated values for the Compensation Resistor to determine the accuracy in non-ideal conditions. We also want to find where the overshoot falls out of spec.

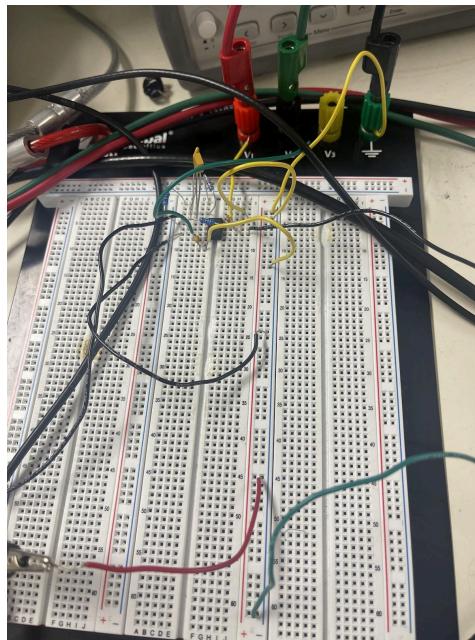


Figure 3.2.1: Breadboard Circuit with  $R_c = 1.03K\Omega$

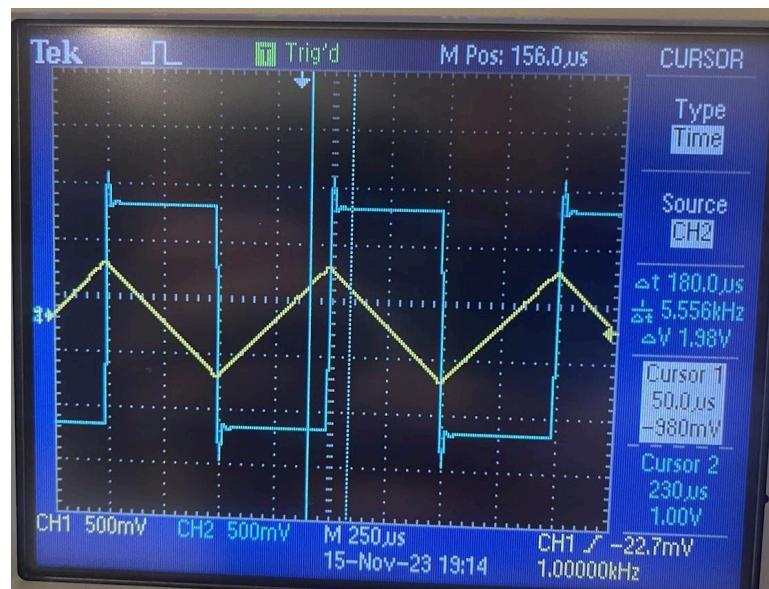


Figure 3.2.2: Oscilloscope Measurements with  $R_c = 1.03K\Omega$

$V_{out}$  (Blue) and  $V_{in}$  (Yellow)

$$V_{OUT}Max = 1.3V$$

### Calculating Overshoot

$$\text{Overshoot \%} = \left( \frac{V_{OUT}Max - V_2}{V_2 - V_1} \right) \times 100$$

$$\text{Overshoot \%} = \left( \frac{1.3 - 1}{1 - (-0.98)} \right) \times 100$$

$$\text{Overshoot \%} = 15.15\%$$

**DOES NOT MEET SPEC**

### Calculating Rise Time

$$V_x = V_1 + 10\% * (V_2 - V_1) = -0.782V$$

$$V_y = V_1 + 90\% * (V_2 - V_1) = 0.802V$$

$$\text{Rise Time} (t_r) = t_2 - t_1$$

$$t_r = (50.3\mu s) - (42.0\mu s)$$

$$t_r = 8.7\mu s$$

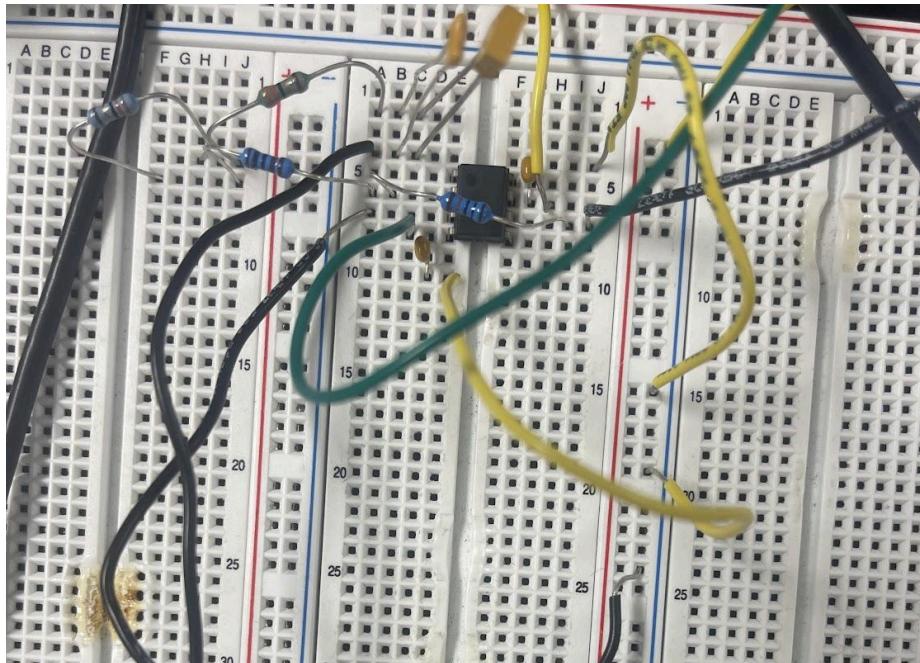


Figure 3.2.3: Breadboard Circuit with  $R_C = 1.06K\Omega$

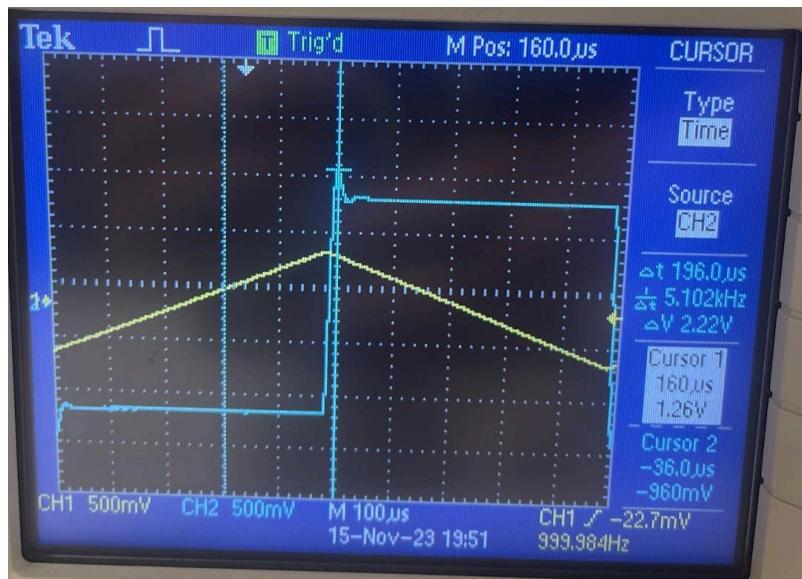


Figure 3.2.4: Oscilloscope Measurements with  $R_C = 1.06K\Omega$

$V_{out}$  (Blue) and  $V_{in}$  (Yellow)

$$V_{OUT} Max = 1.3V$$

### Calculating Overshoot

$$\text{Overshoot \%} = \left( \frac{V_o Max - V_2}{V_2 - V_1} \right) \times 100$$

$$\text{Overshoot \%} = \left( \frac{1.28 - 1}{1 - (-0.96)} \right) \times 100$$

$$\text{Overshoot \%} = 14.286\%$$

**DOES MEET SPEC**

### Calculating Rise Time

$$V_x = V_1 + 10\% * (V_2 - V_1) = -0.762V$$

$$V_y = V_1 + 90\% * (V_2 - V_1) = 0.822V$$

$$\text{Rise Time } (t_r) = t_2 - t_1$$

$$t_r = (151\mu s) - (142\mu s)$$

$$t_r = 9\mu s$$

$R_c$ Value ( $\Omega$ )	Overshoot (%)	Rise Time ( $\mu s$ )
1.03k	15.15%	8.7
1.6k	14.286%	9

Figure 3.2.5: Table of Measured Rc Values

### Part 3)

For this part we will repeat the process as Part 2, except using a Compensation Capacitor instead of a resistor.

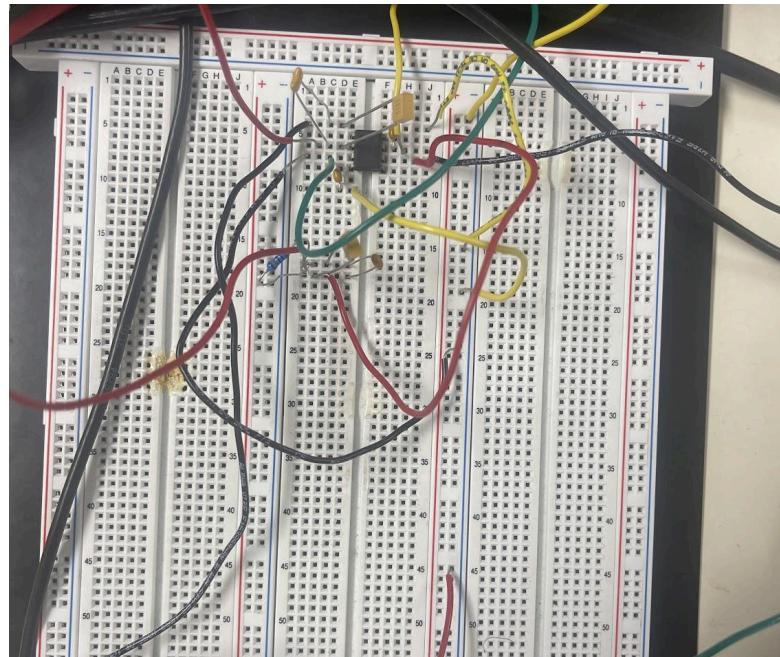


Figure 3.3.1: Breadboard Circuit with a Compensation Capacitor



Figure 3.3.2: Oscilloscope Measurements with  $C_c = 515\text{pF}$

$V_{out}$  (Blue) and  $V_{in}$  (Yellow)

$$V_{OUT} Max = 1.3V$$

### **Calculating Overshoot**

$$\text{Overshoot \%} = \left( \frac{V_o Max - V_2}{V_2 - V_1} \right) \times 100$$

$$\text{Overshoot \%} = \left( \frac{1.28 - 1}{1 - (-0.96)} \right) \times 100$$

$$\text{Overshoot \%} = 14.286\%$$

**NO OVERSHOOT**

### **Calculating Rise Time**

$$V_x = V_1 + 10\% * (V_2 - V_1) = -0.762V$$

$$V_y = V_1 + 90\% * (V_2 - V_1) = 0.822V$$

$$\text{Rise Time} (t_r) = t_2 - t_1$$

$$t_r = (151\mu s) - (142\mu s)$$

$$t_r = 9 \mu s$$

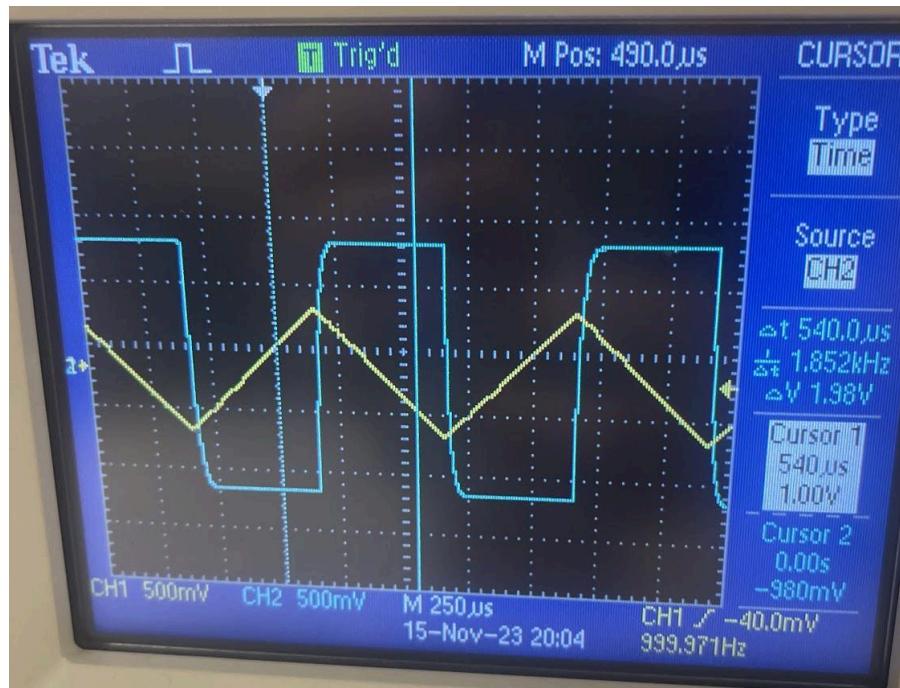


Figure 3.3.3: Oscilloscope Measurements with  $C_c = 170\text{pF}$

No Overshoot

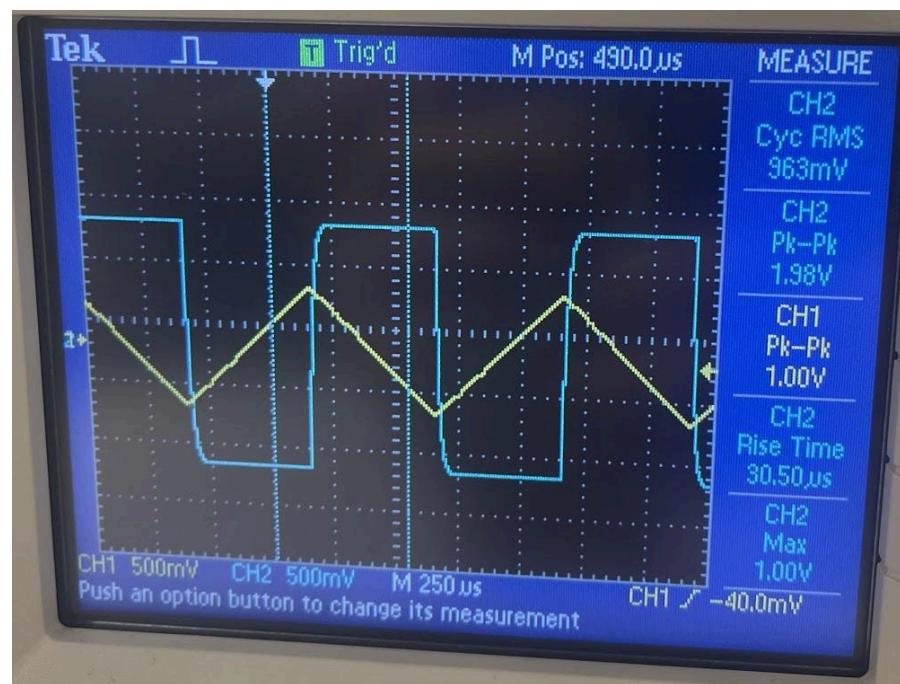


Figure 3.3.4: Oscilloscope Measurements with  $C_c = 150\text{pF}$

No Overshoot

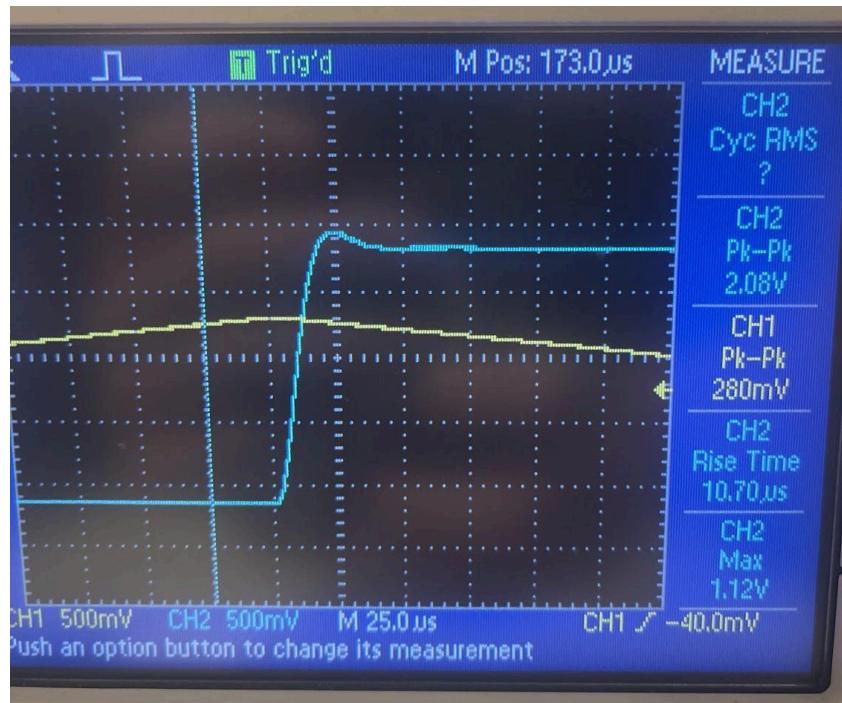


Figure 3.3.5: Oscilloscope Measurements with  $C_c = 68pF$

Overshoot = 12%

$$t_r = 10.7 \mu\text{s}$$

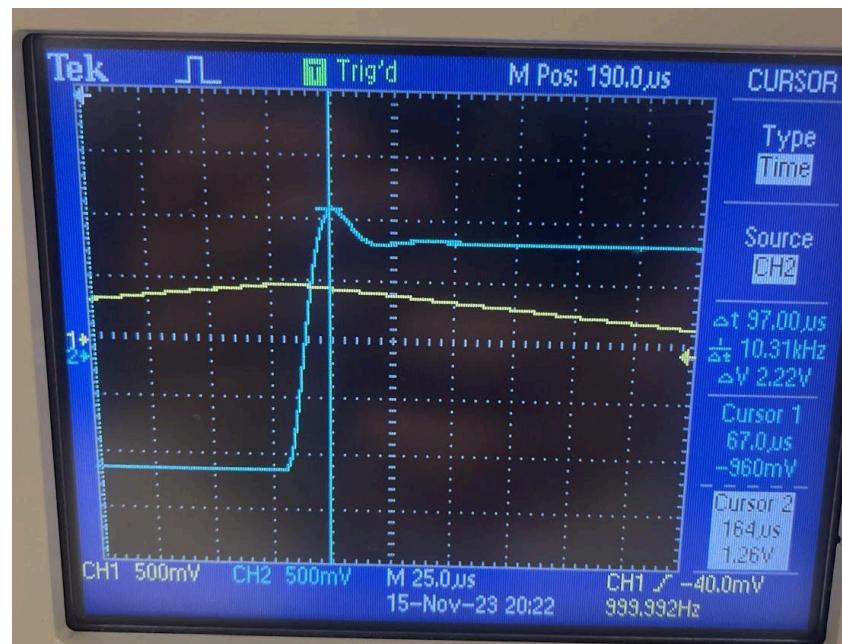


Figure 3.3.6: Oscilloscope Measurements with  $C_c = 51pF$

Overshoot = 13.2%

$$t_r = 9.4 \mu\text{s}$$

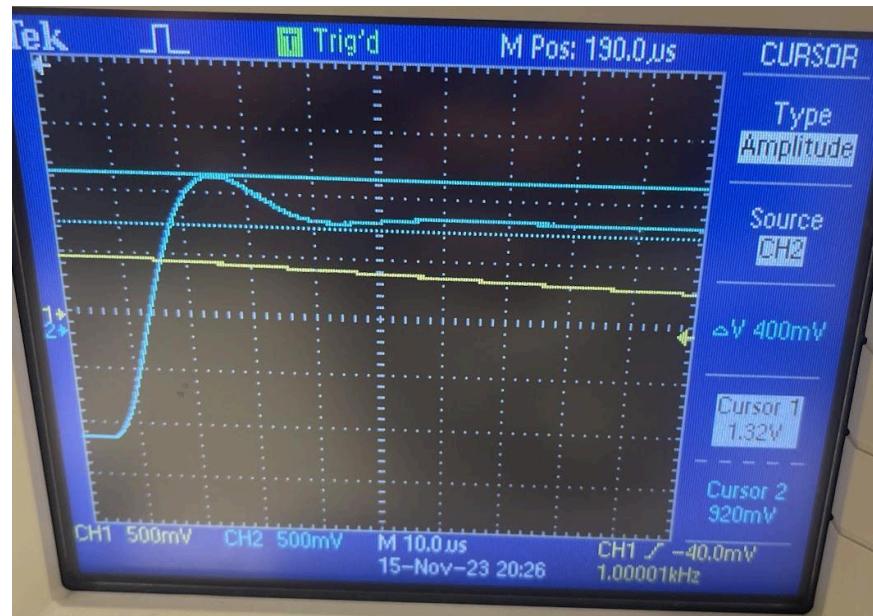


Figure 3.3.7: Oscilloscope Measurements with  $C_c = 47pF$

Overshoot = 16.3 %

$$t_r = 8.7 \mu s$$



Figure 3.3.8: Oscilloscope Measurements with  $C_c = 50.2pF$

Overshoot = 14.2%

$$t_r = 9.2 \mu s$$

$C_c$ Value (pF)	Overshoot (%)	Rise Time $t_r$ (μs)
515	No OS	
170	No OS	
150	No OS	
68	12%	10.7
51	13.2%	9.4
50.2	14.2%	9.2
47	16.3%	8.7

Figure 3.3.9: Table of Measured Cc Values

# Conclusion

The voltage differentiator circuit underwent analysis using equations, Matlab, PSpice, and practical circuit setups. The resistor and capacitor values that best met the specifications showed consistency across Matlab, PSpice, and actual circuit tests. Our analysis revealed that the simplified op-amp model is generally effective, although it has its limitations. During circuit simulation, we noted discrepancies due to the operational amplifier's inherent inconsistencies not fully captured by our simplified model. Nonetheless, it proved useful for initial estimations in our filter design. In the actual filter implementation, our results deviated from theoretical predictions, possibly due to additional impedances on the breadboard and the use of a simplified model in our calculations. We observed that the step response and PSpice simulations did not fully align with real-world behavior; notably, there was a consistent overshoot stabilizing at a value approximately 15% higher than expected. This led to the necessity of adjusting the compensation impedance, opting for higher resistance or lower capacitance. For future experiments, extending our simulations over longer durations could yield more accurate insights for practical implementation.

# MATLAB Code

## Part 1) System Level Design

### 1C

```
s = tf('s')
G1 = 2*pi*3e6; r = 100e3; c= 5e-9;
tau = r*c;
T = G1 / (s*(1+s*tau));
figure (1);
%bode(T, {100,1e6}),
%margin(T);
H = T/(1+T);
%step(H, 1e-3);
stepinfo(H)
```

### 1D (w/ RC)

```
Rc = 1030;
T = G1*(1 + s*Rc*c) / (s*(1 + s*c*(r+Rc)));
%bode(T, {100,1e6});
%margin(T);
H = T/(1+T);
%step(H, 1e-3);
stepinfo(H)
```

### 1D (w/ CC)

```
Cc = 5.155e-11
T = G1*(1 + s*Cc*r) / (s*(1 + s*r*(c+Cc)));
%bode(T, {100,1e6});
%margin(T);
H = T/(1+T);
%step(H, 1e-3);
%stepinfo(H)
```

### 1E

```
Rc = 1.885e3;
T = G1*(1 + s*Rc*c) / (s*(1 + s*c*(r+Rc)));
bode(T, {100,1e6});
margin(T);
H = T/(1+T);
step(H, 1e-3);
stepinfo(H)
```